


# The Junction Field Effect Transistor (JFET)

# FET ( The Field Effect Transistor)


## Few important advantages of FET over conventional Transistors

1. Unipolar device i. e. operation depends on only one type of charge carriers ( $h$  or  $e$ )
2. Voltage controlled Device (gate voltage controls drain current)
3. Very high input impedance ( $\approx 10^9$ - $10^{12} \Omega$ )
4. Source and drain are interchangeable in most Low-frequency applications
5. Low Voltage Low Current Operation is possible (Low-power consumption)
6. Less Noisy as Compared to BJT
7. No minority carrier storage (Turn off is faster)
8. Self limiting device
9. Very small in size, occupies very small space in ICs
10. Low voltage low current operation is possible in MOSFETS
11. Zero temperature drift of out put is possible

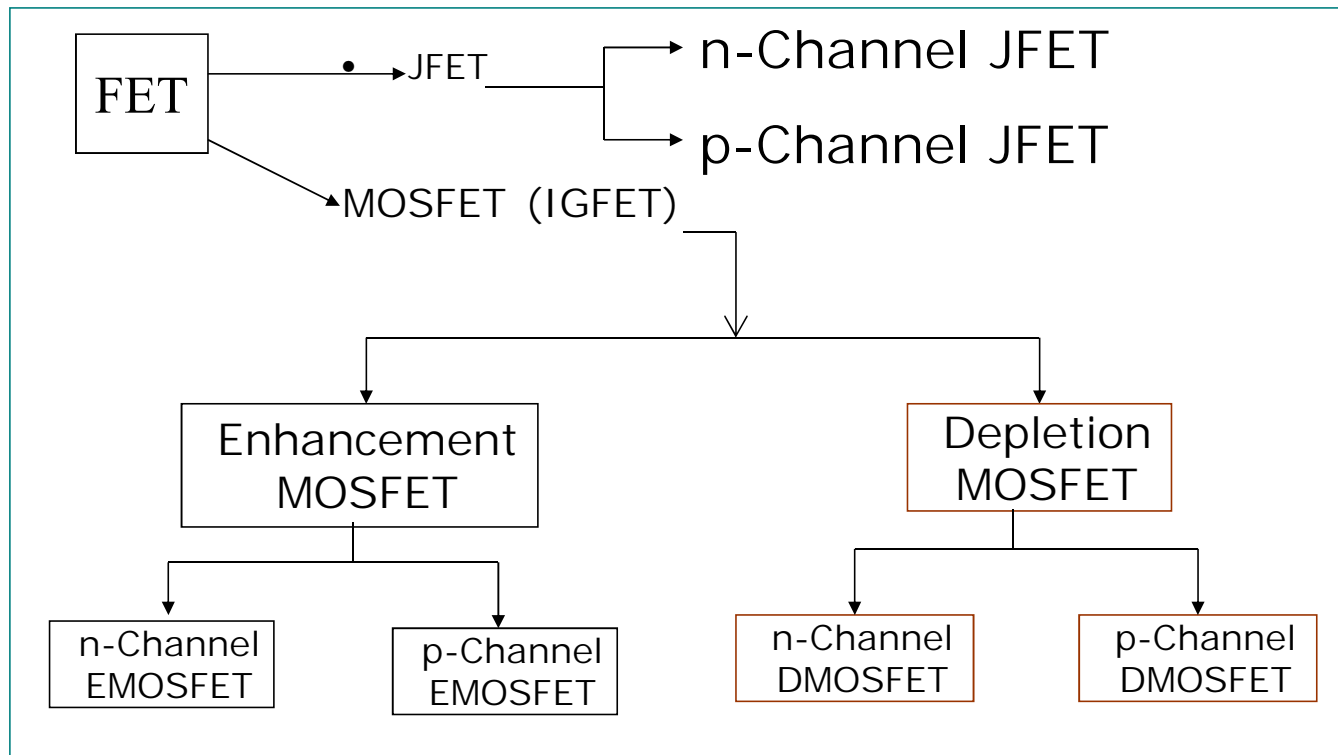
## Types of Field Effect Transistors (The Classification)


 
# The Junction Field Effect Transistor (JFET)




(a) Simplified physical structure

 


(b) Circuit symbol

Figure: n-Channel JFET.


# SYMBOLS

 

n-channel JFET

 


n-channel JFET  
Offset-gate symbol

 


p-channel JFET


# Biassing the JFET

 

(a) Simplified physical structure

 


(b) Circuit symbol

 

**Figure:** *n*-Channel JFET and Biasing Circuit.

## Operation of JFET at Various Gate Bias Potentials

 

**Figure:** The nonconductive depletion region becomes broader with increased reverse bias.  
(Note: The two gate regions of each FET are connected to each other.)

## Output or Drain ( $V_D$ - $I_D$ ) Characteristics of n-JFET

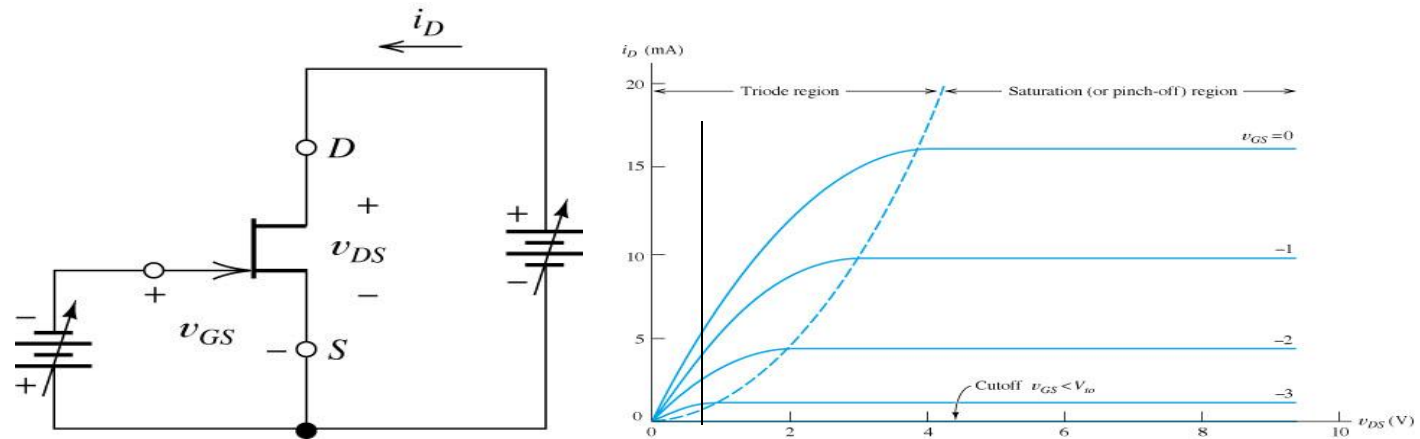


Figure: Circuit for drain characteristics of the  $n$ -channel JFET and its Drain characteristics.

**Non-saturation (Ohmic) Region:**

$$\longrightarrow V_{DS} < (V_{GS} - V_P)$$

The drain current is given by

$$I_{DS} = \frac{2 I_{DSS}}{V_P^2} \left[ (V_{GS} - V_P) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

**Saturation (or Pinchoff) Region:**

$$\longrightarrow V_{DS} \geq (V_{GS} - V_P)$$

$$I_{DS} = \frac{I_{DSS}}{V_P^2} \left[ (V_{GS} - V_P)^2 \right] \quad \text{and} \quad I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

Where,  $I_{DSS}$  is the short circuit drain current,  $V_P$  is the pinch off voltage



## Simple Operation and Break down of n-Channel JFET


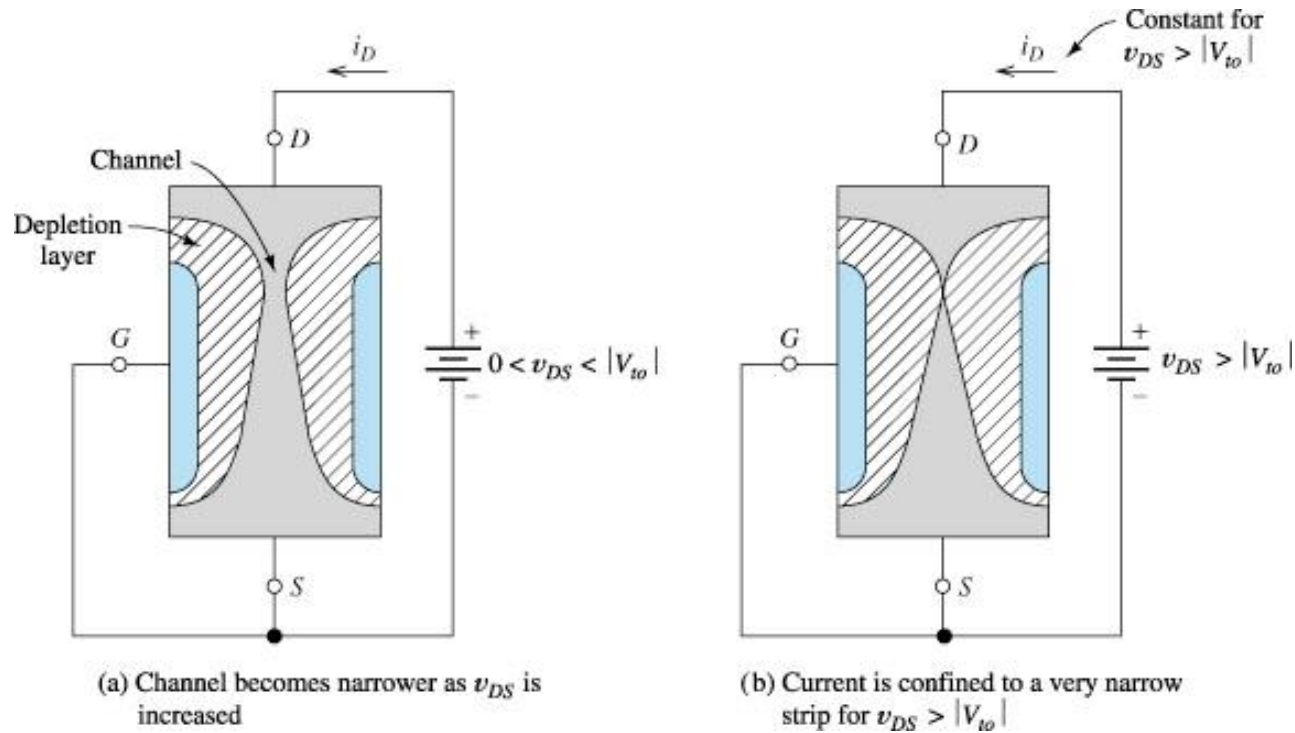



Figure: n-Channel FET for  $v_{GS} = 0$ .

## N-Channel JFET Characteristics and Breakdown

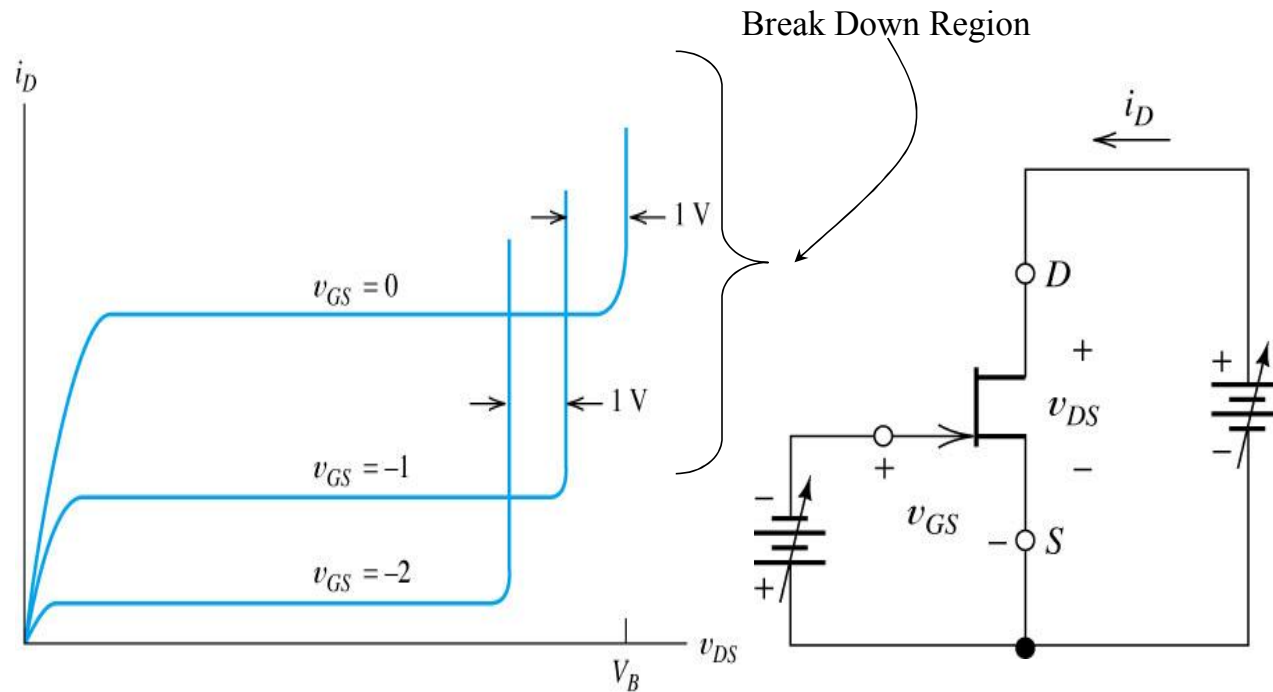

**Figure:** If  $v_{DG}$  exceeds the breakdown voltage  $V_B$ , drain current increases rapidly.

## $V_D$ - $I_D$ Characteristics of FET

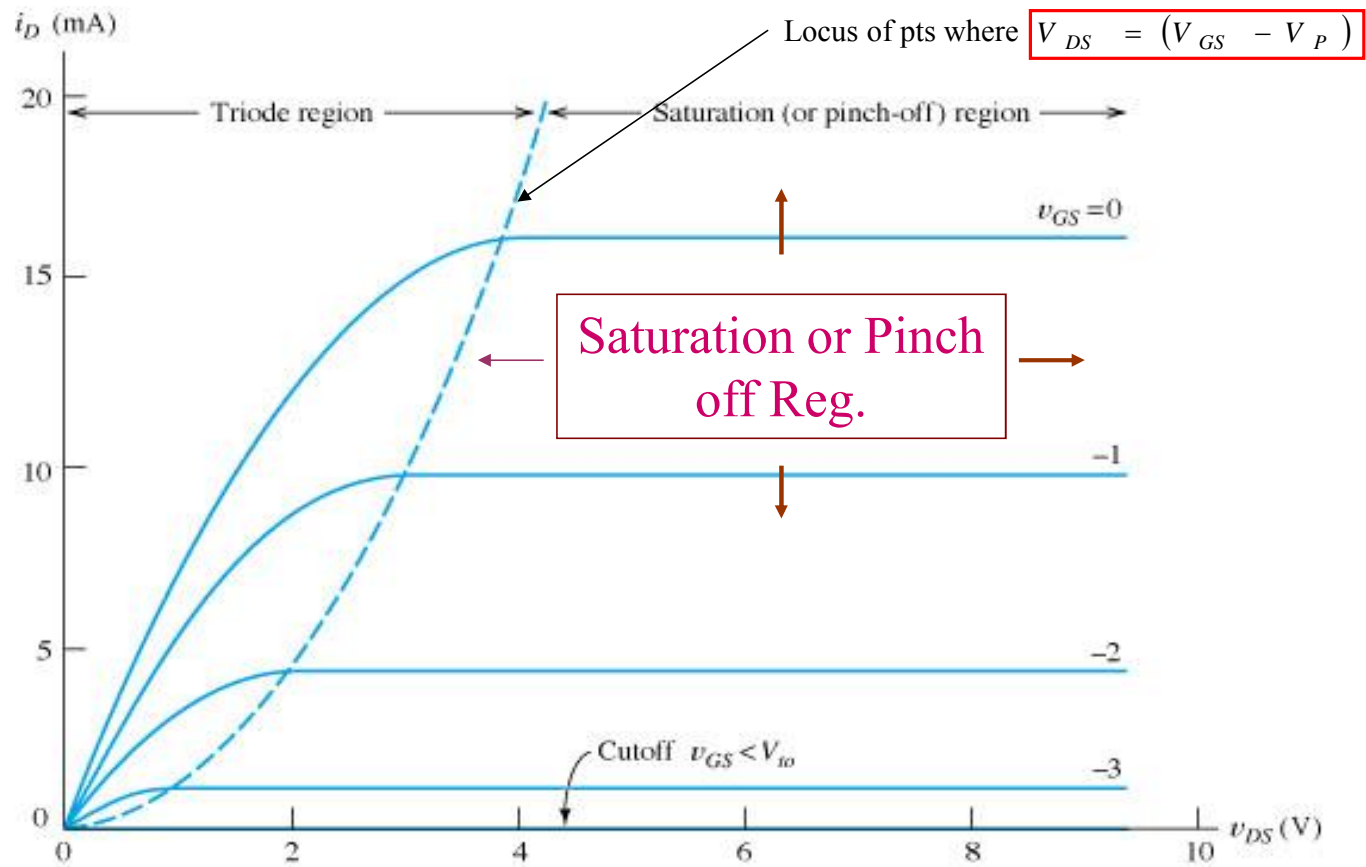

## The Transfer (Mutual) Characteristics of n-Channel JFET


 


Figure: Transfer (or Mutual) Characteristics of n-Channel JFET
 
# The JFET Transfer Curve

This graph shows the value of  $I_D$  for a given value of  $V_{GS}$




## Biasing Circuits used for JFET

- Fixed bias circuit
- Self bias circuit
- Potential Divider bias circuit

## JFET (n-channel) Biasing Circuits

Fixed-bias  
[JFET or D-MOSFET]

 

← For Fixed Bias Circuit

Applying KVL to gate circuit we get

$$V_{GG} = I_G R_G + V_{GS} = V_{GS} = \text{Fixed}, \because I_G = 0$$


and

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\text{and } V_{DS} = V_{DD} - I_{DS} R_D$$

Where,  $V_p = V_{GS\text{-off}}$  &  $I_{DSS}$  is Short ckt.  $I_{DS}$

 Self-bias  
bypassed  $R_S$   
[JFET or D-MOSFET]




← For Self Bias Circuit

$$V_{GS} + I_{DS} R_S = 0$$

$$\therefore I_{DS} = -\frac{V_{GS}}{R_S}$$

## JFET Biasing Circuits Cont.

Gate Bias: or Fixed Bias Ckt.

 

Since  $I_G = 0$ ,

$$V_{GS} = V_{GG}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2$$


- Example: Determine the Q-point values for the gate biasing circuit if  $V_{GG} = -0.5 \text{ V}$ ,  $V_{GS(off)} = -7 \text{ V}$ ,  $I_{DSS} = 9 \text{ mA}$ ,  $V_{DD} = 5 \text{ V}$  and  $R_D = 500 \Omega$ .

$$I_D = (9 \text{ mA}) \left(1 - \frac{-0.5}{-7}\right)^2$$

$$= 7.76 \text{ mA}$$

$$V_{DS} = 5 - (7.76 \text{ mA})(500)$$


$$= 1.12 \text{ V}$$

 



## JFET Self (or Source) Bias Circuit

Self bias:

 

Since  $I_G = 0$ ,  $V_G = 0$

$$V_S = I_D R_S \quad I_D = \frac{-V_{GS}}{R_S}$$


$$V_{GS} = -I_D R_S$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S)$$

$$\text{and } I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\therefore I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 = -\frac{V_{GS}}{R_S}$$

 - Example: Determine the Q-point values for the self biasing circuit if  $V_{GS(off)} = -8 \text{ V}$ ,  $I_{DSS} = 16 \text{ mA}$ ,  $V_{DD} = 10 \text{ V}$ ,  $R_D = 500 \text{ } \Omega$ ,  $R_G = 1 \text{ M}\Omega$  and  $R_S = 500 \text{ } \Omega$ .



$$I_D = 6 \text{ mA}$$


$$V_{DS} = 10 - (6 \text{ mA})(500 + 500) = 4 \text{ V}$$

$$I_{DSS} \left[ 1 - 2 \frac{V_{GS}}{V_P} + \left( \frac{V_{GS}}{V_P} \right)^2 \right] + \frac{V_{GS}}{R_S} = 0$$

This quadratic equation can be solved for  $V_{GS}$  &  $I_{DS}$

## The Potential (Voltage) Divider Bias

Voltage-divider bias:

 

Since  $I_G = 0$ ,

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$I_D = \frac{V_S}{R_S} = \frac{V_G - V_{GS}}{R_S}$$

$$\therefore I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 - \frac{V_G - V_{GS}}{R_S} = 0$$

Solving this quadratic equation gives  $V_{GS}$  and  $I_{DS}$

The method used to plot the dc bias line for the voltage-divider bias is as follows:

1. Plot the transconductance curve for the specific JFET.
2. Calculate  $V_G$ .
3. Plot  $V_G$  on the positive x-axis.


4. Solve for  $I_D$  using

$$I_D = \frac{V_G}{R_S}$$

5. Plot  $I_D$  found in (4) on the y-axis.

6. Extend the line to intersect the transconductance curve to obtain the Q-point values.
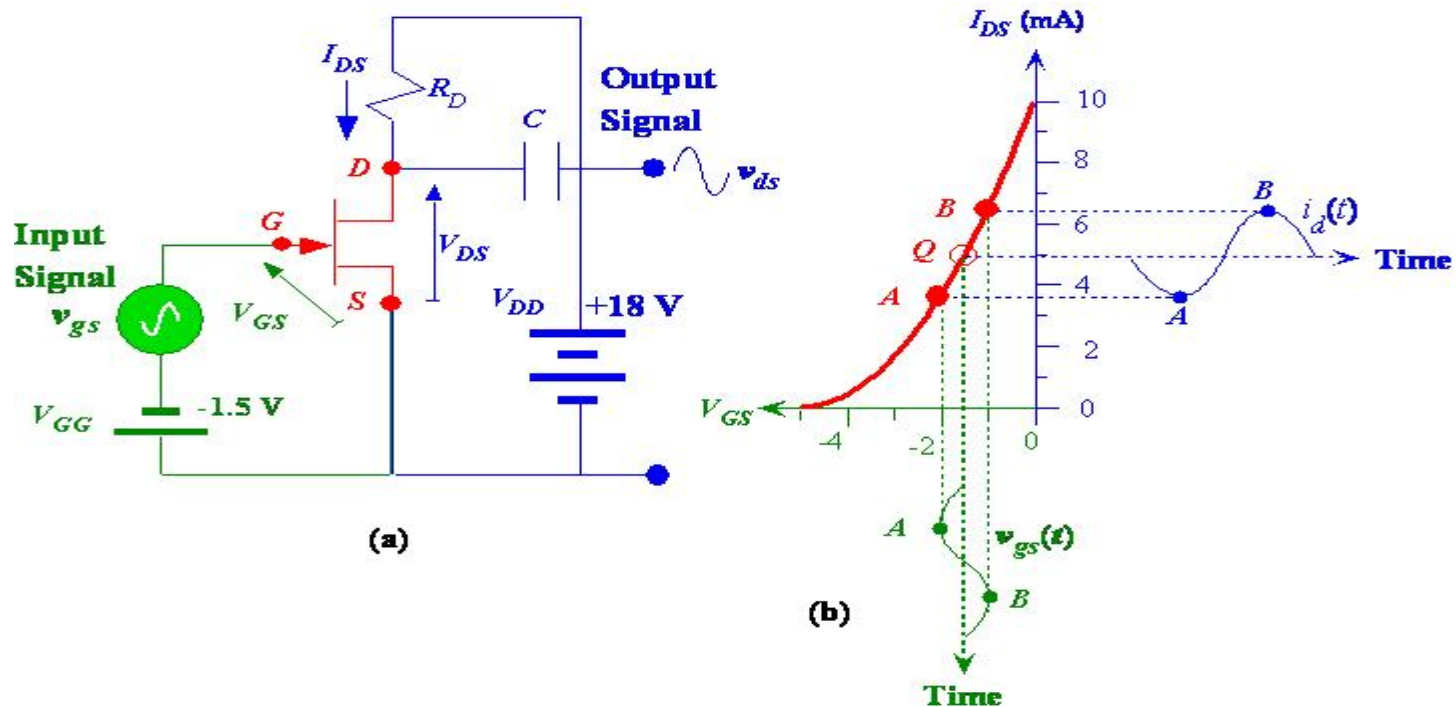
## A Simple CS Amplifier and Variation in $I_{DS}$ with $V_{gs}$



(a) Common source (CS) ac amplifier using a JFET.

(b) Explanation of how  $I_D$  is modulated by the signal  $v_{gs}$  in series with the dc bias voltage  $V_{GG}$



# FET Mid-frequency Analysis:

A common source (CS) amplifier is shown to the right.

The mid-frequency circuit is drawn as follows:

- the coupling capacitors ( $C_i$  and  $C_o$ ) and the bypass capacitor ( $C_{SS}$ ) are short circuits
- short the DC supply voltage (superposition)
- replace the FET with the hybrid- $\pi$  model

  The resulting mid-frequency circuit is shown below.



Analysis of the CS mid-frequency circuit above yields:

$$A_{vi} = \frac{v_o}{v_i} = -g_m R'_L, \text{ where } R'_L = r_d \parallel R_D \parallel R_L$$

$$A_{vs} = \frac{v_o}{v_s} = A_{vi} \left[ \frac{Z_i}{R_s + Z_i} \right]$$

$$Z_i = \frac{v_i}{i_i} = R_{Th}, \text{ where } R_{Th} = R_1 \parallel R_2$$

$$A_I = \frac{i_o}{i_i} = A_{vi} \left[ \frac{Z_i}{R_L} \right]$$

$$Z_o = \left. \frac{v_o}{i_o} \right|_{\text{seen by } R_L} = r_d \parallel R_D$$

$$A_p = \frac{p_o}{p_i} = A_{vi} A_I$$



# FET Mid-frequency Analysis:

A common source (CS) amplifier is shown to the right.

The mid-frequency circuit is drawn as follows:

- the coupling capacitors ( $C_i$  and  $C_o$ ) and the bypass capacitor ( $C_{SS}$ ) are short circuits
- short the DC supply voltage (superposition)
- replace the FET with the hybrid- $\pi$  model

  The resulting mid-frequency circuit is shown below.



Analysis of the CS mid-frequency circuit above yields:

$$A_{v_i} = \frac{v_o}{v_i} = -g_m R'_L, \text{ where } R'_L = r_d \parallel R_D \parallel R_L$$

$$A_{v_s} = \frac{v_o}{v_s} = A_{v_i} \left[ \frac{Z_i}{R_s + Z_i} \right]$$

$$Z_i = \frac{v_i}{i_i} = R_{Th}, \text{ where } R_{Th} = R_1 \parallel R_2$$

$$A_1 = \frac{i_o}{i_i} = A_{v_i} \left[ \frac{Z_i}{R_L} \right]$$

$$Z_o = \left. \frac{v_o}{i_o} \right|_{\text{seen by } R_L} = r_d \parallel R_D$$

$$A_p = \frac{P_o}{P_i} = A_{v_i} A_1$$

## Procedure: Analysis of an FET amplifier at mid-frequency:

- 1) **Find the DC Q-point.** This will insure that the FET is operating in the saturation region and these values are needed for the next step.
- 2) **Find  $g_m$ .** If  $g_m$  is not specified, calculate it using the DC values of  $V_{GS}$  as follows:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{2I_{DSS}}{V_P} (V_{GS} - V_P) \quad (\text{for JFET's and DM MOSFET's})$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = K (V_{GS} - V_T) \quad (\text{for EM MOSFET's})$$

(Note: Uses DC value of  $V_{GS}$ )

- 3) **Calculate the required values (typically  $A_{vi}$ ,  $A_{vs}$ ,  $A_I$ ,  $A_P$ ,  $Z_i$ , and  $Z_o$ .** Use the formulas for the appropriate amplifier configuration (CS, CG, CD, etc).