

COLLEGE OF ENGINEERING & TECHNOLOGY



Department: Computer Engineering

Lecturers: Prof. Dr. Magdy Saeb

Course: Digital Systems Design

Course No.: CC317


Date: June 2005 Time: 120 minutes Grade: 40 Marks

Student Name:
Registration No.:
Department:
Date:
Course Title: Digital Systems Design
Semester:

.....
.....
.....
.....
تصميم النظم الرقمية
.....

إسم الطالب:
رقم التسجيل:
القسم:
تاريخ الإمتحان:
إسم المقرر:
الفترة:

Question No.	Marks
First	
Second	
Third	
Fourth	
Fifth	
Sixth	
Total	

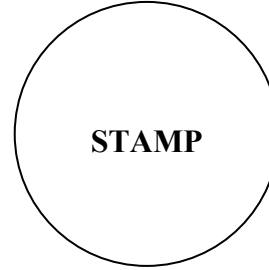

Marks in Letter	Grade	Signature

- *Solve all of the following problems,*
- *Maximum grade is 100 points.*

Problem 1:
(On Codes)

12 Points

- 1.1 Using Hamming code for error detection and correction encode character 'A' which ASCII code is 41_H.
- 1.2 For the BCD arithmetic code 7421, encode the decimal number 953. Discuss the power consumption of this code as compared to other arithmetic codes that you have studied.

Problem 2:
(On Quine-McCluskey)

12 Points

Find the internal representation of the Quine-McCluskey data structure of the following expression:

$$P1 = X15.X12'.X10'.X9.X4'.X1.X0$$

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
																t.
																f.

Problem 3:
(On Static Hazards)

12 Points

Find the static hazard, if any, for the following logic expression:

$$F = WXZ' \cdot YZ \cdot X'Y'$$


Problem 4:
(On VHDL and decoders)

12 Points

Complete the following VHDL code :

```
entity V74x138 is  
    port (    signal G2A_L, G2B_L: STD_LOGIC;  
            signal G1: STD_LOGIC;  
            signal Y: STD_LOGIC_VECTOR (0 to 7);  
            signal A: STD_LOGIC_VECTOR(2 downto 0));
```

```
architecture V74x138_b of V74x138 is  
    signal Y_s : STD_LOGIC_Vector (0 to 7);  
    signal G2A:STD_LOGIC;  
    signal G2B:STD_LOGIC;  
begin  
    G2A <= not G2A_L;  
    G2B <= not G2B_L;  
    Y_L <= not Y;  
with A select Y_s .....?  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When ".....?",  
    ".....?" When others;  
Y <= Y_s when ( G1 and G2A and G2B) = '1' else ".....?";  
end V74x138-b;
```

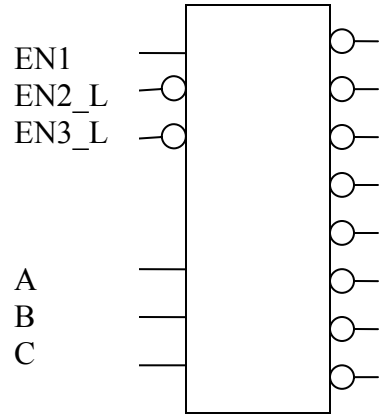

74x138 decoder

Hint: Refer to Figure shown below for the 74x138 decoder symbol.

Problem 5:
(On Switching algebra and notation (T/F))

12 Points

Indicate whether each of the following equations is true or false. That is, mark “T” if the left-hand-side equals the right-hand side for every possible combination of the input variables, otherwise mark “F”.

___ (a) $(W \cdot X + Y' + Z)' = (W' + X') \cdot Y \cdot Z'$

___ (b) $W' \oplus X' \oplus Y' \oplus Z = \Sigma_{WXYZ}(0,3,5,6,9,10,12,15)$


___ (c) $\Sigma_{WXYZ}(1,6,11,15) = W' \cdot X' \cdot Y' \cdot Z + W' \cdot X \cdot Y \cdot Z' + W \cdot X' \cdot Y \cdot Z + W \cdot X \cdot Y \cdot Z'$

___ (d) $\Sigma_{WXYZ}(1,6,11,15) = W' \cdot X' \cdot Y' \cdot Z + W' \cdot X \cdot Y \cdot Z' + W \cdot Y \cdot Z$

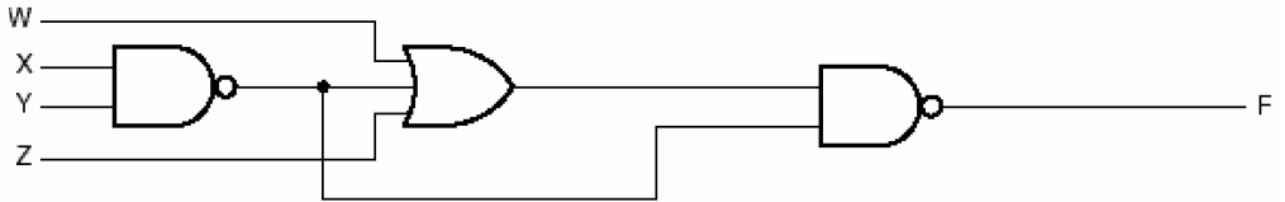Problem 6:
(On Combinational Circuit Analysis)

12 Points

Write a logic expression for the output F of the circuit below as a function of the circuit inputs (W , X , Y , and Z). Derive the expression directly from the structure of the circuit; do not simplify.



$F =$ _____


Problem 7:
(On Combinational Circuit Minimization)

12 Points

- a) Fill in the Karnaugh map and find a minimal sum of products expression for the function $F = \Sigma w,x,y,z(2,6,7,8,9,10,11,15)$.
 b) How many additional product terms are in the complete sum for this logic function?

Answer:

- a) $F =$ _____
 b) No. of additional product terms = _____

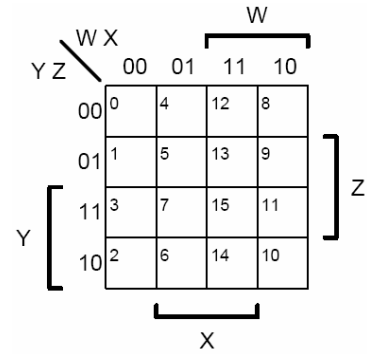

Problem 8:
(On the “BUT” Gate)

12 Points

Y1 is 1 if A1 and B1 are both 1 *but* A2 and B2 are not both 1;

Y2 is 1 if A2 and B2 are both 1 *but* A1 and B1 are not both 1;

Write the truth table for the following two logic statements.

Problem 9:
(On Application Design)


12 Points

We would like to design a robot maneuvering control system. The robot is equipped with high quality sensors, a front, right and left object detector. This detector sets the “LeftWall” signal, if there is a wall to his left, sets the “RightWall” signal, if there is a wall to his right and finally sets the “FrontWall” signal, if there a wall in front of him. The robot has a motor that enables him to rotate 90° to the left when setting the “TurnLeft” signal, 90° to the right when setting the “TurnRight” signal, and 180° to the right when setting the “TurnAround” signal. You are not allowed to set any two or three signals of the above motor-signals simultaneously. The robot can walk to the front when setting the “Walk” signal. Imagine the robot being inside a room and you want to design a control system for him to get him out of the room. Write the suitable logic equations for each motor-signal that will drive the robot outside the room.

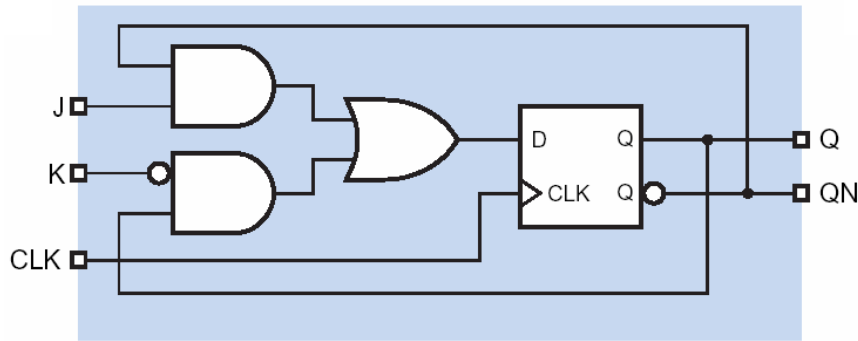
**Problem 10:
(On Flip-Flops)**

12 Points

Write the expected output Q and QN in the below truth table. Moreover, draw the output signal Q in the below timing diagram.



J	K	CLK	Q	QN
x	x	0		
x	x	1		
0	0			
0	1			
1	0			
1	1			

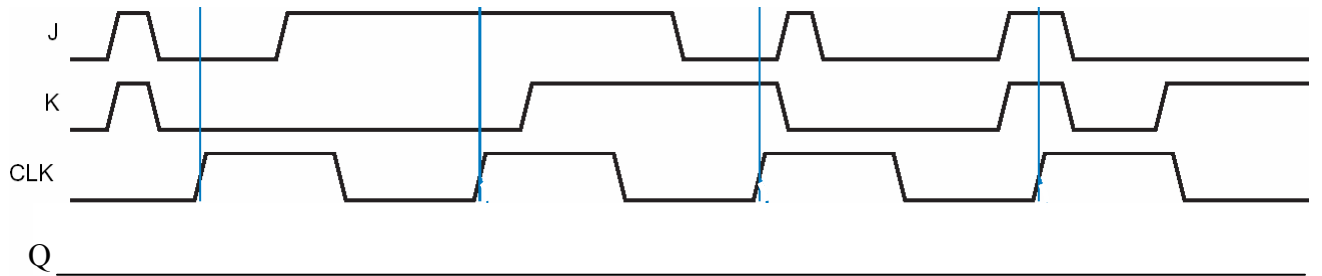

Problem 11:
(On PLD)

12 points

Find the logic expression realized by the following PLD:

