

Fig. 8-1 ASM Chart Elements

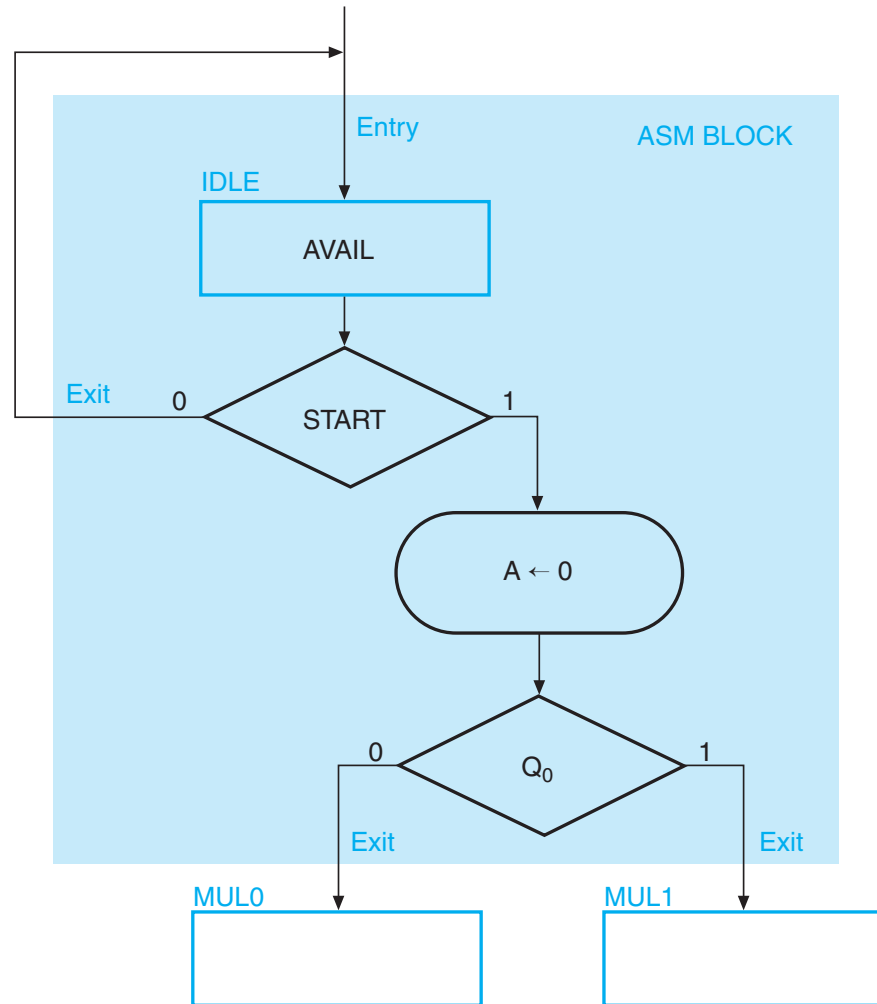


Fig. 8-2 ASM Block

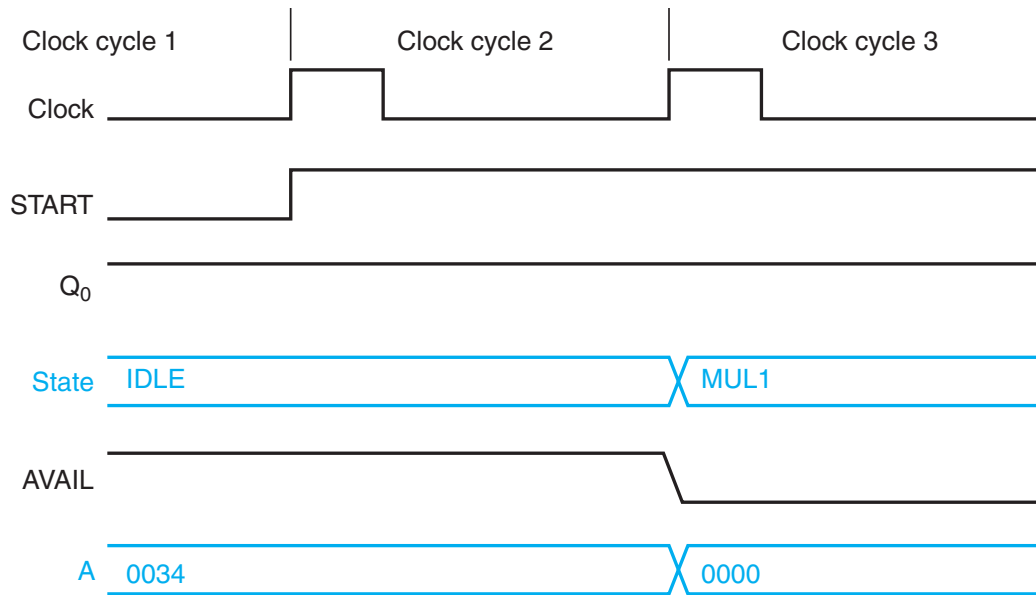


Fig. 8-3 ASM Timing Behavior

23	10111	Multiplicand
<u>19</u>	<u>10011</u>	Multiplier
	10111	
	10111	
	00000	
	00000	
	<u>10111</u>	
437	110110101	Product

Fig. 8-4 Hand Multiplication Example

23	10111	Multiplicand
<u>19</u>	<u>10011</u>	Multiplier
	00000	Initial partial product
	<u>10111</u>	Add multiplicand, since multiplier bit is 1
	10111	Partial product after add and before shift
	010111	Partial product after shift
	<u>10111</u>	Add multiplicand, since multiplier bit is 1
	1000101	Partial product after add and before shift ^a
	1000101	Partial product after shift
	01000101	Partial product after shift
	001000101	Partial product after shift
	<u>10111</u>	Add multiplicand, since multiplier bit is 1
	110110101	Partial product after add and before shift
437	0110110101	Product after final shift

a. Note that overflow temporarily occurred.

Fig. 8-5 Hardware Multiplication Example

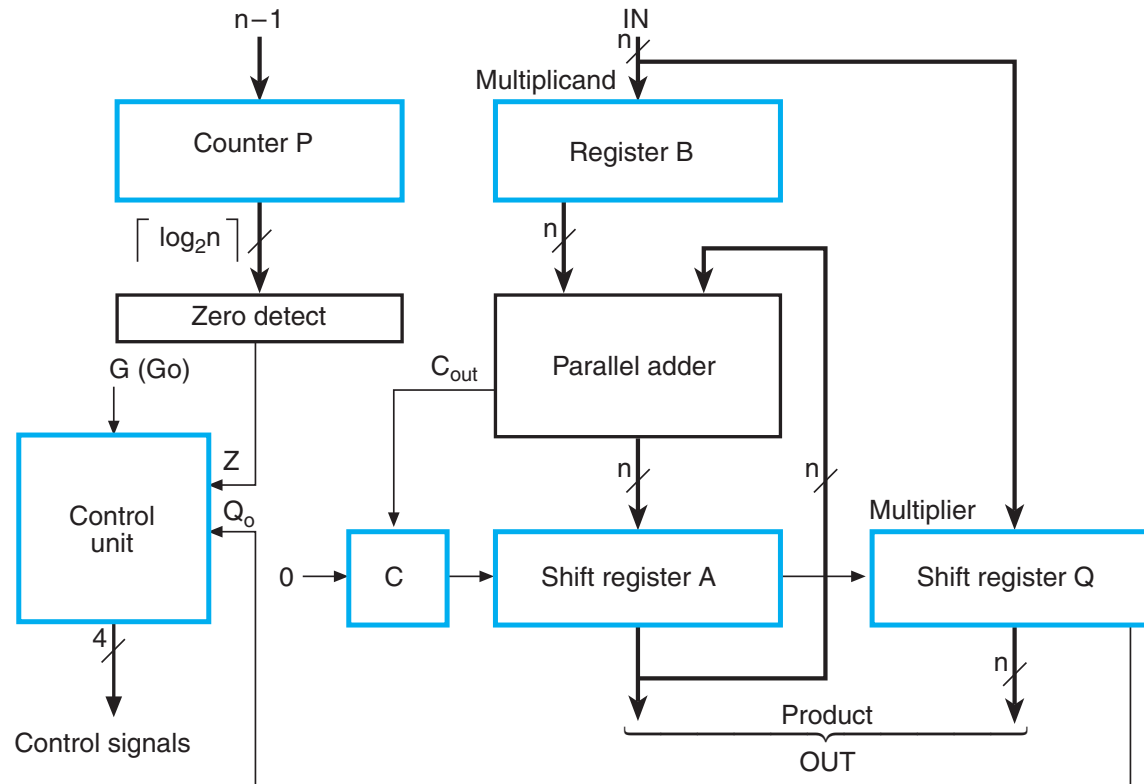


Fig. 8-6 Block Diagram for Binary Multiplier

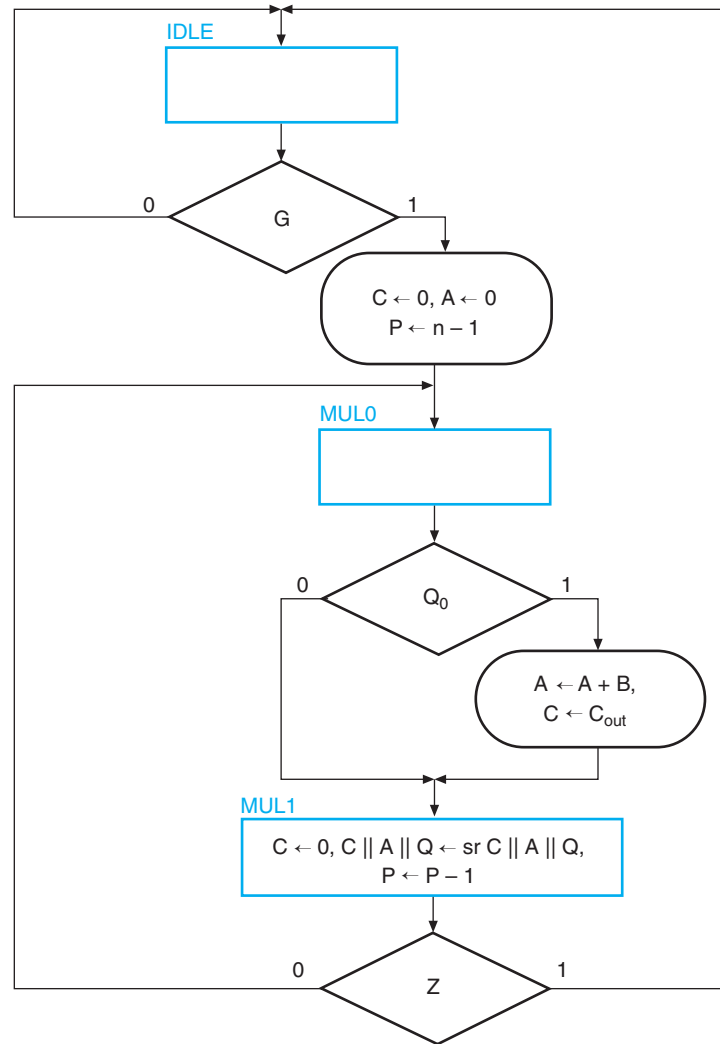


Fig. 8-7 ASM Chart for Binary Multiplier

TABLE 8-1
Control Signals for Binary Multiplier

Block Diagram Module	Microoperation	Control Signal Name	Control Expression
Register <i>A</i> :	$A \leftarrow 0$	Initialize	$IDLE \cdot G$
	$A \leftarrow A + B$	Load	$MUL0 \cdot Q_0$
	$C \ A \ Q \leftarrow sr \ C \ A \ Q$	Shift_dec	MUL1
Register <i>B</i> :	$B \leftarrow IN$	Load_B	LOADB
Flip-Flop <i>C</i> :	$C \leftarrow 0$	Clear_C	$IDLE \cdot G + MUL1$
	$C \leftarrow C_{out}$	Load	—
Register <i>Q</i> :	$Q \leftarrow IN$	Load_Q	LOADQ
	$C \ A \ Q \leftarrow sr \ C \ A \ Q$	Shift_dec	—
Counter <i>P</i> :	$P \leftarrow n - 1$	Initialize	—
	$P \leftarrow P - 1$	Shift_dec	—

Table 8-1 Control Signals for Binary Multiplier

 


Fig. 8-8 Sequencing Part of ASM Chart for the Binary Multiplier

TABLE 8-2
State Table for Sequence Register and Decoder Part
of Multiplier Control Unit

Present state			Inputs		Next state		Decoder Outputs		
Name	M ₁	M ₀	G	Z	M ₁	M ₀	IDLE	MUL0	MUL1
IDLE	0	0	0	×	0	0	1	0	0
	0	0	1	×	0	1	1	0	0
MUL0	0	1	×	×	1	0	0	1	0
MUL1	1	0	×	0	0	1	0	0	1
	1	0	×	1	0	0	0	0	1
—	1	1	×	×	×	×	×	×	×

Table 8-2 State Table for Sequence Register and Decoder Part of Multiplier Control Unit


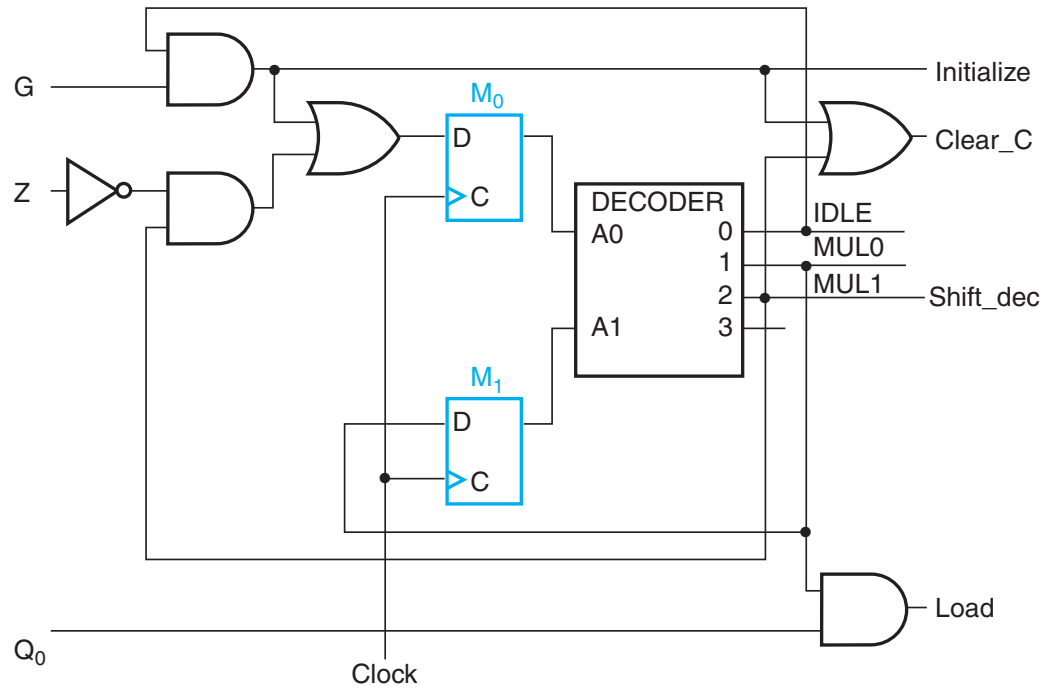


Fig. 8-9 Control Unit for Binary Multiplier Using a Sequence Register and a Decoder

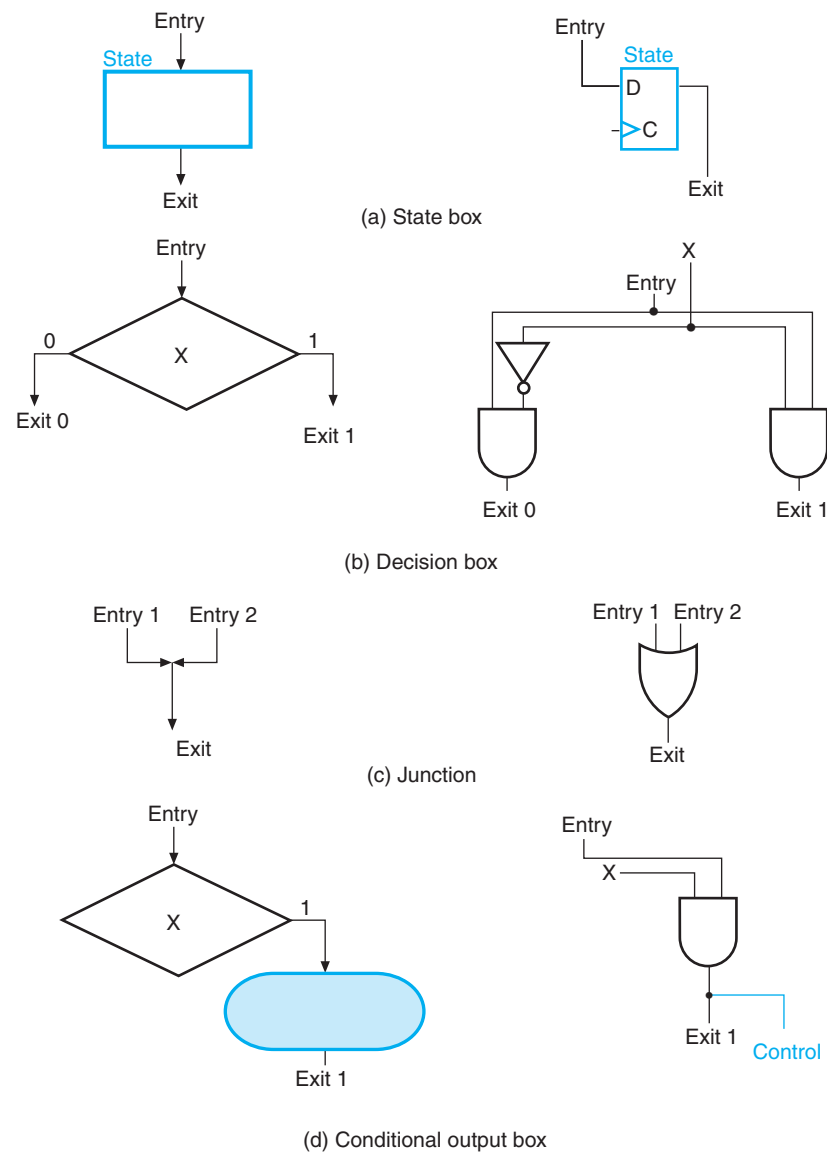

(a) State box

(b) Decision box

(c) Junction

(d) Conditional output box

Fig. 8-10 Transformation Rules for Control Unit with One Flip-Flop per State

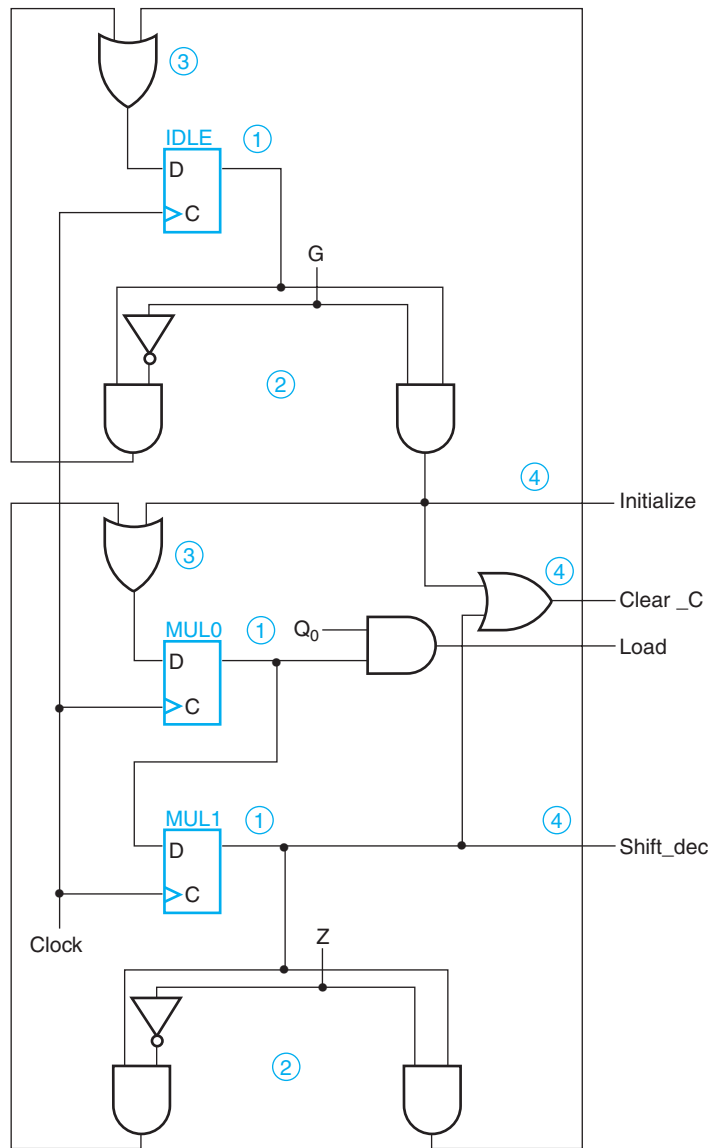


Fig. 8-11 Control Unit with One Flip-Flop per State for the Binary Multiplier

```

-- Binary Multiplier with n = 4: VHDL Description
-- See Figures 8-6 and 8-7 for block diagram and ASM Chart
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;
entity binary_multiplier is
    port(CLK, RESET, G, LOADB, LOADQ: in std_logic;
         MULT_IN: in std_logic_vector(3 downto 0);
         MULT_OUT: out std_logic_vector(7 downto 0));
end binary_multiplier;

architecture behavior_4 of binary_multiplier is
    type state_type is (IDLE, MUL0, MUL1);
    signal state, next_state : state_type;
    signal A, B, Q: std_logic_vector(3 downto 0);
    signal P: std_logic_vector(1 downto 0);
    signal C, Z: std_logic;
begin
    Z <= P(1) NOR P(0);
    MULT_OUT <= A & Q;

    state_register: process (CLK, RESET)
    begin
        if (RESET = '1') then
            state <= IDLE;
        elsif (CLK'event and CLK = '1') then
            state <= next_state;
        end if;
    end process;

    next_state_func: process (G, Z, state)
    begin
        case state is
            when IDLE =>
                if G = '1' then
                    next_state <= MUL0;
                else
                    next_state <= IDLE;
                end if;
            when MUL0 =>
                next_state <= MUL1;
            when MUL1 =>
                if Z = '1' then
                    next_state <= IDLE;
                else
                    next_state <= MUL0;
                end if;
        end case;
    end process;
end behavior_4;

```

Fig. 8-12 VHDL Description of a Binary Multiplier

```

        end case;
    end process;

datapath_func: process (CLK)
    variable CA: std_logic_vector(4 downto 0);
begin
    if (CLK'event and CLK = '1') then
        if LOADB = '1' then
            B <= MULT_IN;
        end if;
        if LOADQ = '1' then
            Q <= MULT_IN;
        end if;
        case state is
            when IDLE =>
                if G = '1' then
                    C <= '0';
                    A <= "0000";
                    P <= "11";
                end if;
            when MUL0 =>
                if Q(0) = '1' then
                    CA := ('0' & A) + ('0' & B);
                else
                    CA := C & A;
                end if;
                C <= CA(4);
                A <= CA(3 downto 0);
            when MUL1 =>
                C <= '0';
                A <= C & A(3 downto 1);
                Q <= A(0) & Q(3 downto 1);
                P <= P - "01";
            end case;
        end if;
    end process;
end behavior_4;

```

Fig. 8-13 VHDL Description of a Binary Multiplier (Continued)

```

// Binary Multiplier with n = 4: Verilog Description
// See Figures 8-6 and 8-7 for block diagram and ASM Chart

module binary_multiplier_v (CLK, RESET, G, LOADB, LOADQ,
    MULT_IN, MULT_OUT);
input CLK, RESET, G, LOADB, LOADQ;
input [3:0] MULT_IN;
output [7:0] MULT_OUT;
reg [1:0] state, next_state, P;
parameter IDLE = 2'b00, MUL0 = 2'b01, MUL1 = 2'b10;
reg [3:0] A, B, Q;
reg C;
wire Z;

assign Z = ~| P;
assign MULT_OUT = {A,Q};

//state register
always@(posedge CLK or posedge RESET)
begin
    if (RESET == 1)
        state <= IDLE;
    else
        state <= next_state;
end

//next state function
always@(G or Z or state)
begin
    case (state)
        IDLE:
            if (G == 1)
                next_state <= MUL0;
            else
                next_state <= IDLE;
        MUL0:
            next_state <= MUL1;
        MUL1:
            if (Z == 1)
                next_state <= IDLE;
            else
                next_state <= MUL0;
    endcase
end

//datapath function
always@(posedge CLK)

```

Fig. 8-14 Verilog Description of a Binary Multiplier


```

begin
  if (LOADB == 1)
    B <= MULT_IN;
  if (LOADQ == 1)
    Q <= MULT_IN;
  case (state)
    IDLE:
      if (G == 1)
        begin
          C <= 0;
          A <= 4'b0000;
          P <= 2'b11;
        end
    MUL0:
      if (Q[0] == 1)
        {C, A} = A + B;
    MUL1:
      begin
        C <= 1'b0;
        A <= {C, A[3:1]};
        Q <= {A[0], Q[3:1]};
        P <= P - 2'b01;
      end
  endcase
end
endmodule

```

Fig. 8-15 Verilog Description of a Binary Multiplier (Continued)

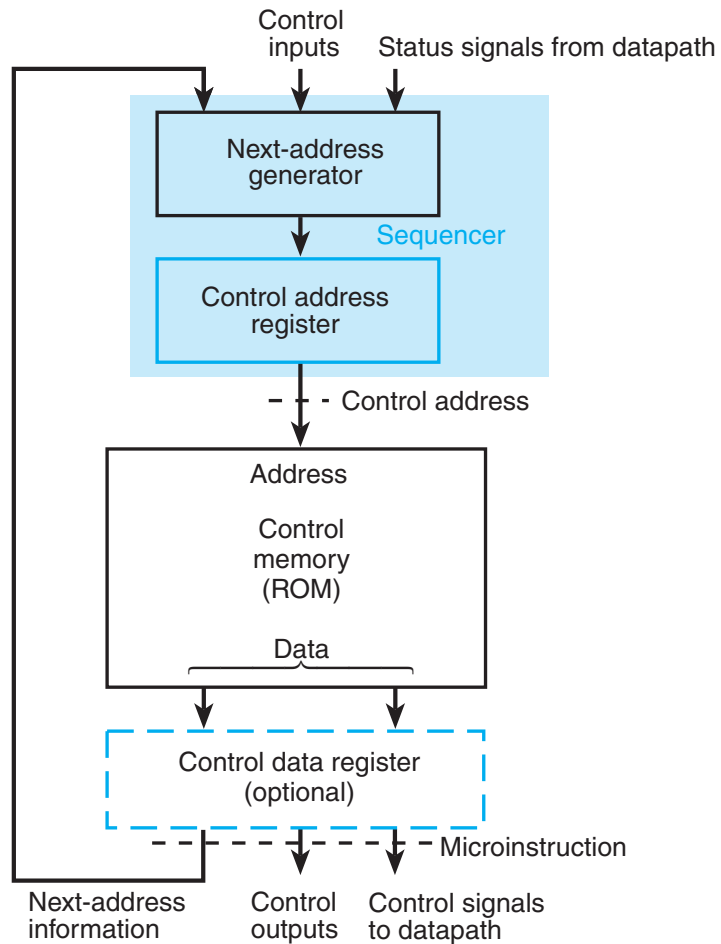


Fig. 8-16 Microprogrammed Control Unit Organization

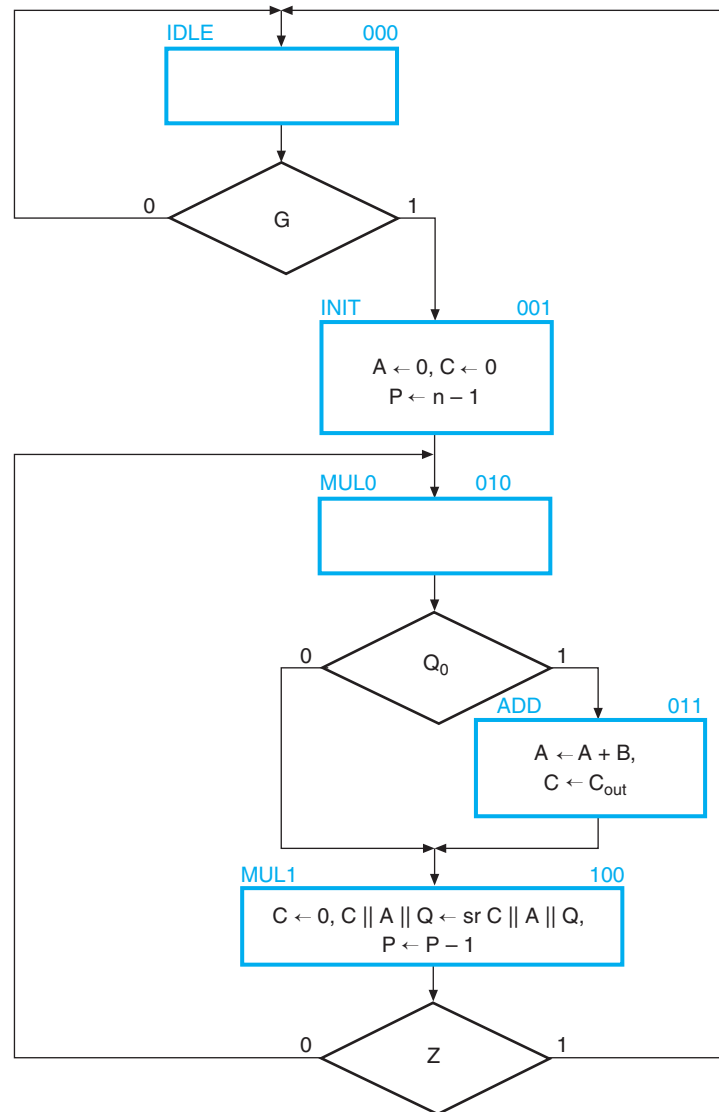


Fig. 8-17 ASM Chart for Microprogrammed Binary Multiplier Control Unit

 


Fig. 8-18 Microinstruction Control Word Format

□ **TABLE 8-3**
Control Signals for Microprogrammed Multiplier Control

Control Signal	Register Transfers	States in Which Signal is Active	Micro-instruction Bit Position	Symbolic Notation
Initialize	$A \leftarrow 0, P \leftarrow n - 1$	INIT	0	IT
Load	$A \leftarrow A + B, C \leftarrow C_{\text{out}}$	ADD	1	LD
Clear_C	$C \leftarrow 0$	INIT, MUL1	2	CC
Shift_dec	$C \parallel A \parallel Q \leftarrow \text{sr } C \parallel A \parallel Q, P \leftarrow P - 1$	MUL1	3	SD

Table 8-3 Control Signals for Microprogrammed Multiplier Control

□ **TABLE 8-4**
SEL Field Definition for Binary Multiplier
Control Sequencing

SEL		
Symbolic notation	Binary Code	Sequencing Microoperations
NXT	00	$CAR \leftarrow NXTADD0$
DG	01	$\overline{G}: CAR \leftarrow NXTADD0$ $G: CAR \leftarrow NXTADD1$
DQ	10	$\overline{Q}_0: CAR \leftarrow NXTADD0$ $Q_0: CAR \leftarrow NXTADD1$
DZ	11	$\overline{Z}: CAR \leftarrow NXTADD0$ $Z: CAR \leftarrow NXTADD1$

Table 8-4 SEL Field Definition for Binary Multiplier Control Sequencing

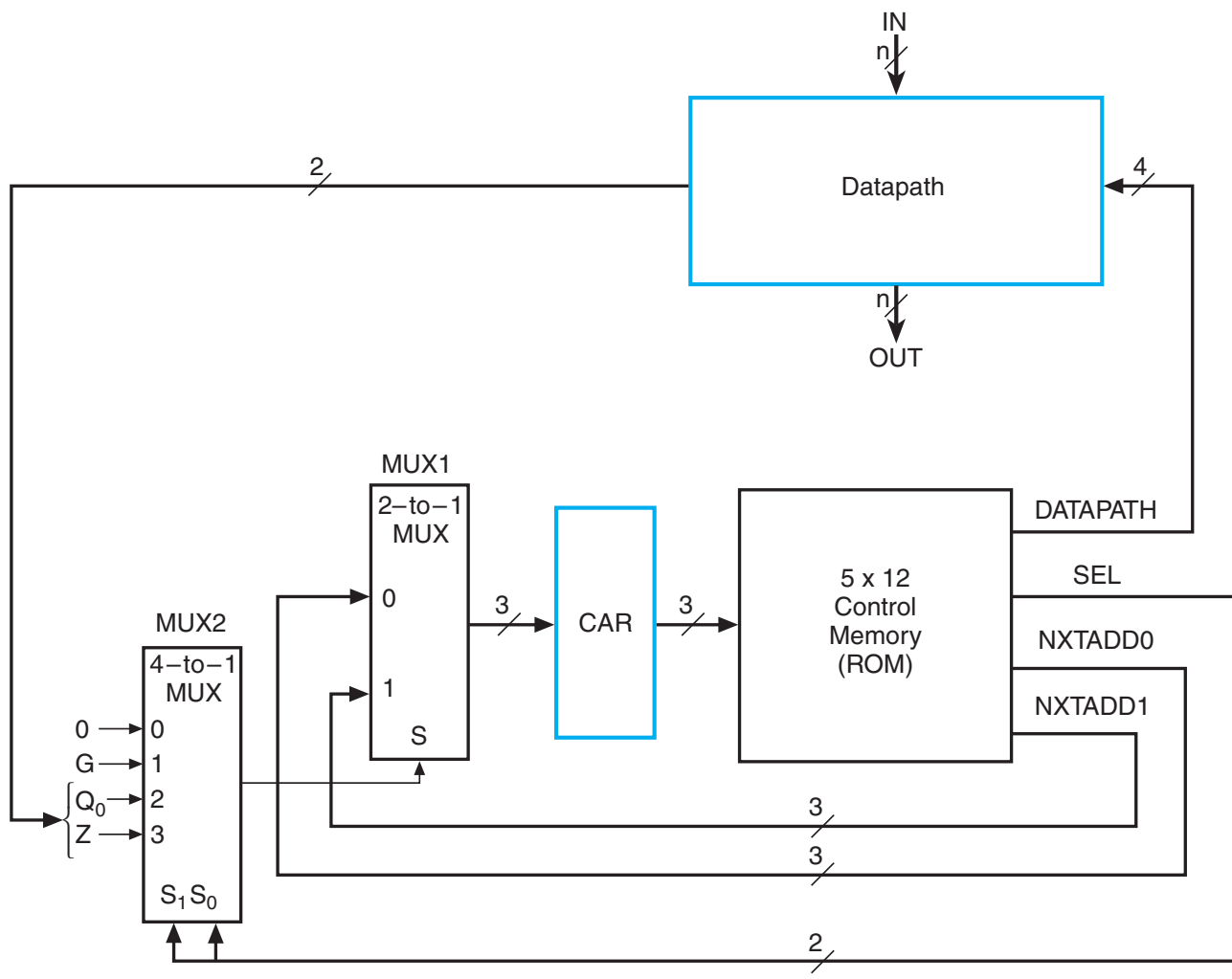


Fig. 8-19 Microprogrammed Control Unit for Multiplier

□ **TABLE 8-5**
Register Transfer Description of Binary Multiplier Microprogram


Address	Symbolic transfer statement
IDLE	$G: CAR \leftarrow \text{INIT}, \bar{G}: CAR \leftarrow \text{IDLE}$
INIT	$C \leftarrow 0, A \leftarrow 0, P \leftarrow n-1, CAR \leftarrow \text{MUL0}$
MUL0	$Q_0: CAR \leftarrow \text{ADD}, \bar{Q}_0: CAR \leftarrow \text{MUL1}$
ADD	$A \leftarrow A + B, C \leftarrow C_{\text{out}}, CAR \leftarrow \text{MUL1}$
MUL1	$C \leftarrow 0, C \ A \ Q \leftarrow \text{sr } C \ A \ Q, Z: CAR \leftarrow \text{IDLE}, \bar{Z}: CAR \leftarrow \text{MUL0},$ $P \leftarrow P - 1$

Table 8-5 Register Transfer Description of Binary Multiplier Microprogram


□ **TABLE 8-6**
Symbolic Microprogram and Binary Microprogram for Multiplier

Address	NXTADD1	NXTADD0	SEL	DATAPATH	Address	NXTADD1	NXTADD0	SEL	DATAPATH
IDLE	INIT	IDLE	DG	None	000	001	000	01	0000
INIT	—	MUL0	NXT	IT, CC	001	000	010	00	0101
MUL0	ADD	MUL1	DQ	None	010	011	100	10	0000
ADD	—	MUL1	NXT	LD	011	000	100	00	0010
MUL1	IDLE	MUL0	DZ	CC, SD	100	000	010	11	1100


Table 8-6 Symbolic Microprogram and Binary Microprogram for Multiplier

 

(a) Register

 

(b) Immediate

 

(c) Jump and Branch

Fig. 8-20 Three Instruction Formats

Decimal address	Memory contents	Decimal opcode	Other specified fields	Operation
25	0000101 001 010 011	5 (Subtract)	DR:1, SA:2 SB:3	$R1 \leftarrow R2 - R3$
35	0100000 000 100 101	32 (Store)	SA:4 SB:5	$M[R4] \leftarrow R5$
45	1000010 010 111 011	66 (Add Immediate)	DR:2 SA:7 OP:3	$R2 \leftarrow R7 + 3$
55	1100011 101 110 100	96 (Branch on zero)	AD: 44 SA:6	If $R6 = 0$, $PC \leftarrow PC - 20$
70	0000000 011 000 000	Data = 192. After execution of instruction in 35, Data = 80.		

Fig. 8-21 Memory Representation of Instructions and Data

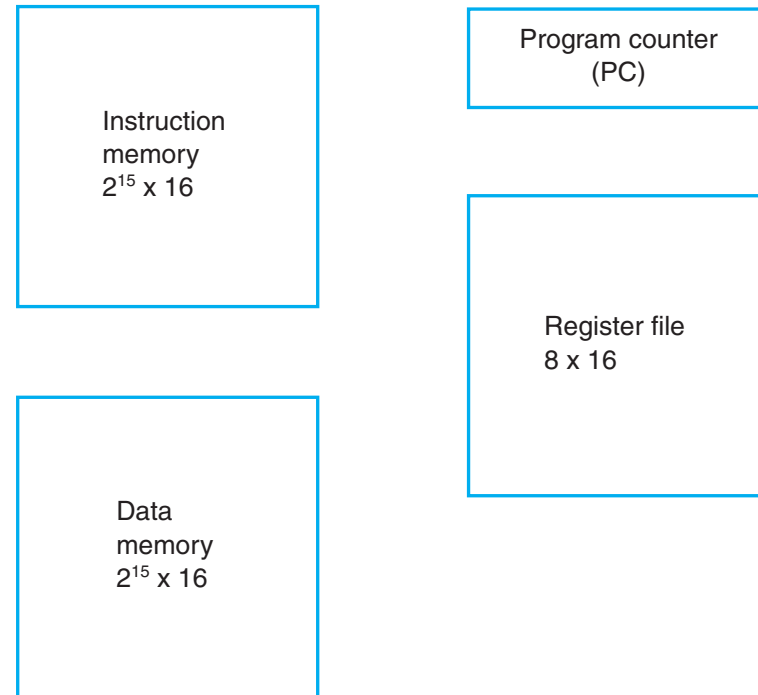


Fig. 8-22 Storage Resource Diagram for a Simple Computer

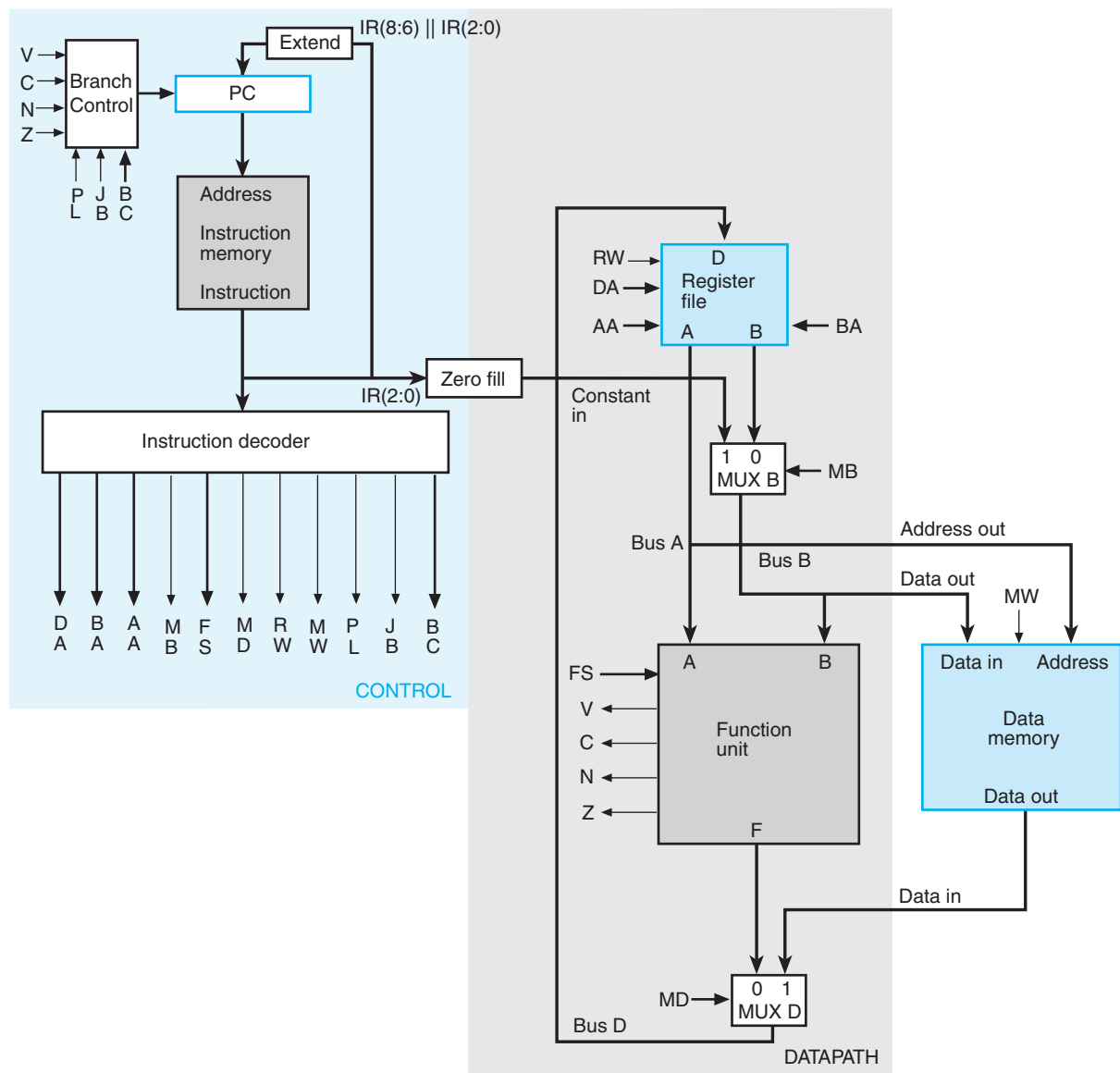


Fig. 8-23 Block Diagram for a Single-Cycle Computer

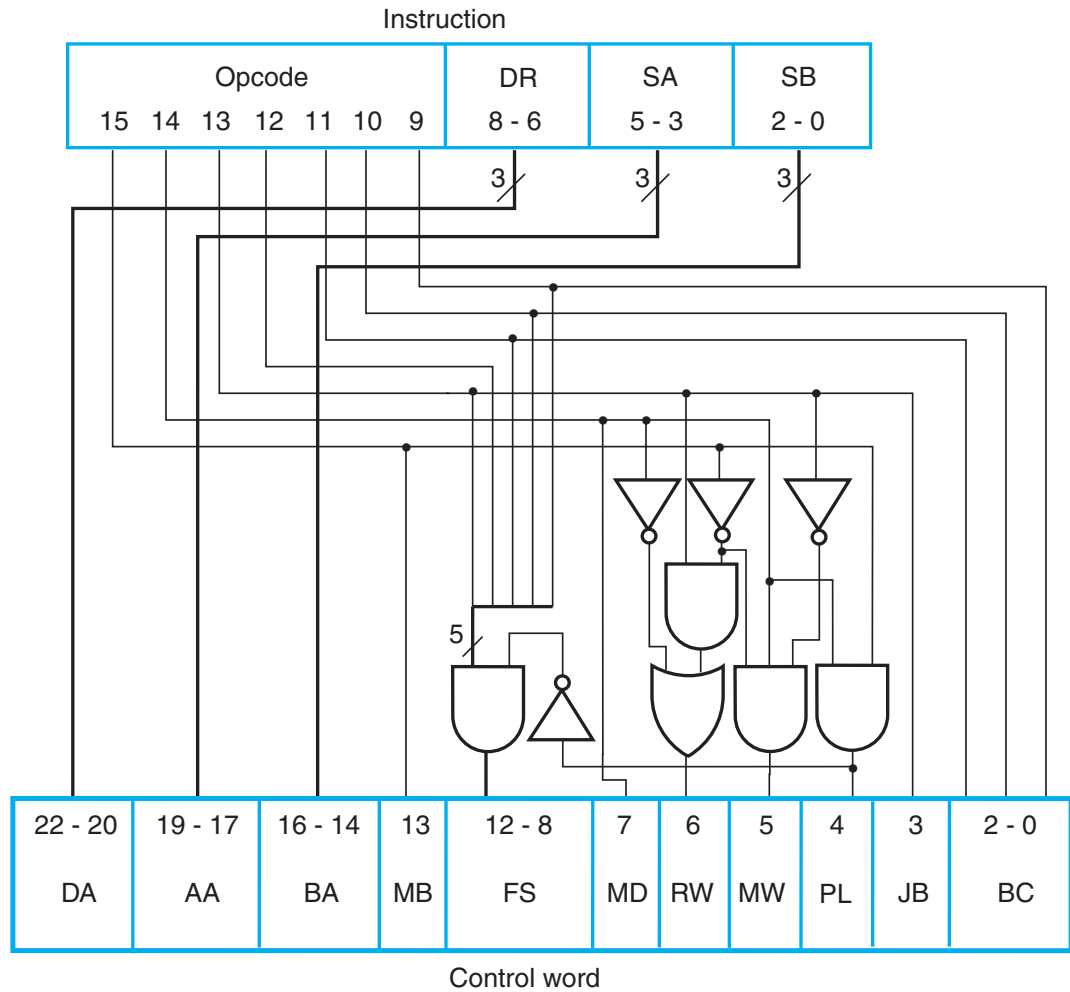


Fig. 8-24 Diagram of Instruction Decoder

TABLE 8-7
Truth Table for Instruction Decoder Logic

Instruction Function Type	Instruction Bits			Control Word Bits					
	Bit 15	Bit 14	Bit 13	MB	MD	RW	MW	PL	JB
ALU function using registers	0	0	0	0	0	1	0	0	X
Shifter function using registers	0	0	1	0	0	1	0	0	X
Memory write using register data	0	1	0	0	X	0	1	0	X
Memory read using register data	0	1	1	0	1	1	0	0	X
ALU operation using a constant	1	0	0	1	0	1	0	0	X
Shifter function using a constant	1	0	1	1	0	1	0	0	X
Conditional Branch	1	1	0	X	X	0	0	1	0
Unconditional Jump	1	1	1	X	X	0	0	1	1

Table 8-7 Truth Table for Instruction Decoder Logic

□ **TABLE 8-8**
Six Instructions for the Single-Cycle Computer

Operation code	Symbolic name	Format	Description	Function	MB	MD	RW	MW	PL	JB
1000010	ADI	Immediate	Add immediate operand	$R[DR] \leftarrow R[SA] + zf I(2:0)$	1	0	1	0	0	0
0110000	LD	Register	Load memory content into register	$R[DR] \leftarrow M[R[SA]]$	0	1	1	0	0	1
0100000	ST	Register	Store register content in memory	$M[R[SA]] \leftarrow R[SB]$	0	1	0	1	0	0
0011000	SL	Register	Shift left	$R[DR] \leftarrow slR[SB]$	0	0	1	0	0	1
0001110	NOT	Register	Complement register	$R[DR] \leftarrow \overline{R[SA]}$	0	0	1	0	0	0
1100000	BRZ	Jump/Branch	If $R[SA] = 0$, branch to $PC + se AD$	If $R[SA] = 0, PC \leftarrow PC + seAD,$ If $R[SA] \neq 0, PC \leftarrow PC + 1$	1	0	0	0	1	0

Table 8-8 Six Instructions for the Single-Cycle Computer

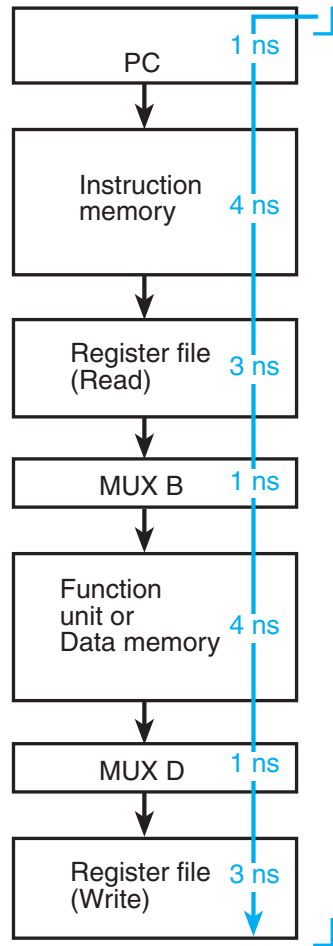


Fig. 8-25 Worst Case Delay Path in Single-Cycle Computer

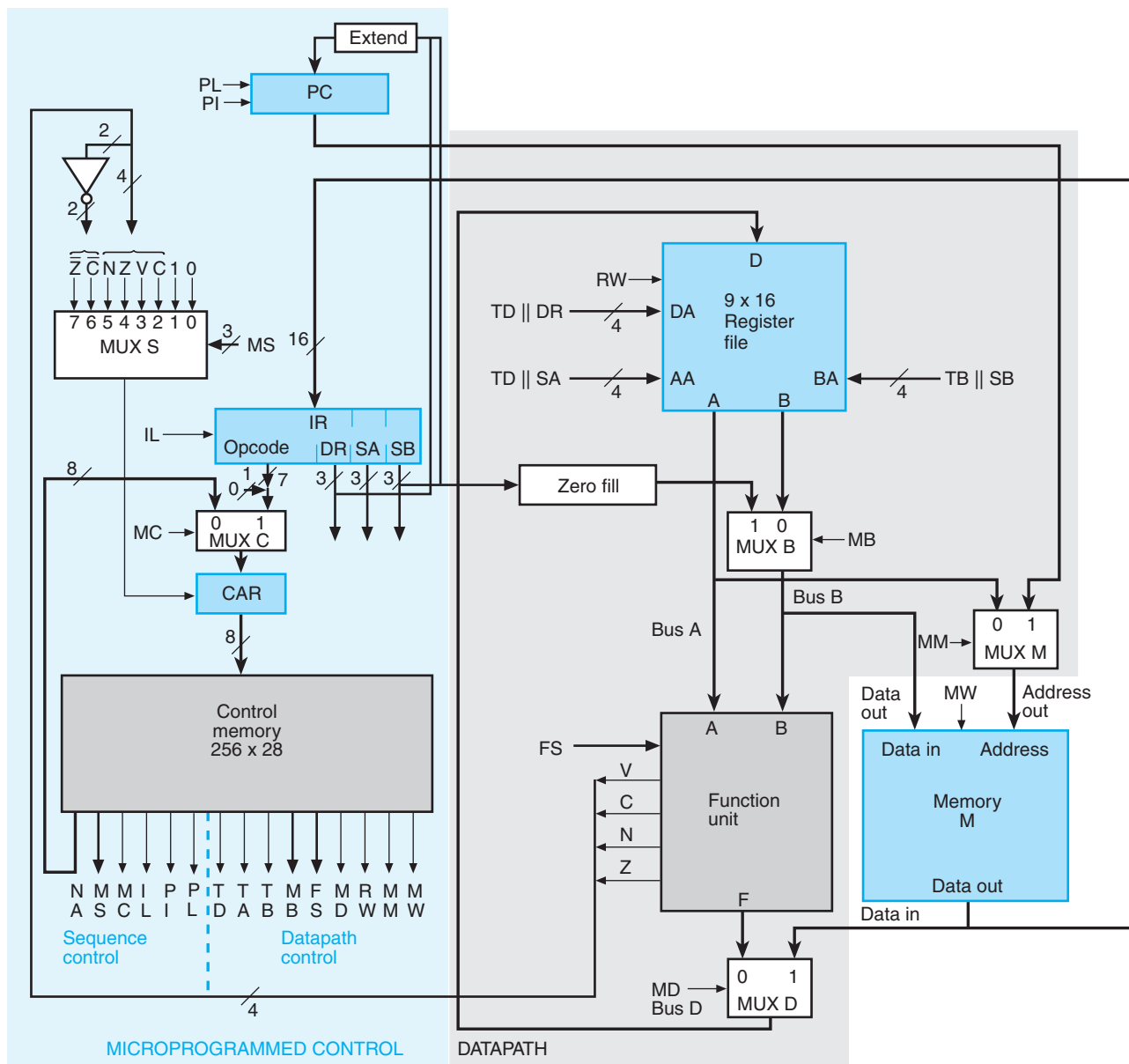


Fig. 8-26 Multiple-Cycle Microprogrammed Computer

 


Fig. 8-27 Format for Microinstruction

□ **TABLE 8-9**
Control Word Information for Datapath

TD	TA	TB	MB		FS		MD	RW		MM	MW	
Select	Select	Select	Select	Code	Function	Code	Select	Function	Select	Function	Code	
$R[DR]$	$R[SA]$	$R[SB]$	Register	0	$F = A$	00000	FnUt	No write (NW)	Address	No write (NW)	0	
$R8$	$R8$	$R8$	Constant	1	$F = A + 1$	00001	Data In	Write (WR)	PC	Write (WR)	1	
					$F = A + B$	00010						
					$F = A + B + 1$	00011						
					$F = A + \overline{B}$	00100						
					$F = A + \overline{B} + 1$	00101						
					$F = A - 1$	00110						
					$F = A$	00111						
					$F = A \wedge B$	01000						
					$F = A \vee B$	01010						
					$F = A \oplus B$	01100						
					$F = \overline{A}$	01110						
					$F = B$	10000						
					$F = \text{sr } B$	10100						
					$F = \text{sl } B$	11000						

Table 8-9 Control Word Information for Datapath

TABLE 8-10
Control Information for Sequence Control Fields

MS			MC		IL		PI		PL		
Action	Symbolic Notation	Code	Select	Symbolic Notation	Action	Symbolic Notation	Action	Symbolic Notation	Action	Symbolic Notation	Code
Increase <i>CAR</i>	CNT	000	NA	NXA	No load	NLI	No load	NLP	No load	NLP	0
Load <i>CAR</i>	NXT	001	Opcode	OPC	Load instr.	LDI	Increase PC	INP	Load PC	LDP	1
If <i>C</i> = 1, load <i>CAR</i> ; else increase <i>CAR</i>	BC	010									
If <i>V</i> = 1, load <i>CAR</i> ; else increase <i>CAR</i>	BV	011									
If <i>Z</i> = 1, load <i>CAR</i> ; else increase <i>CAR</i>	BZ	100									
If <i>N</i> = 1, load <i>CAR</i> ; else increase <i>CAR</i>	BN	101									
If <i>C</i> = 0, load <i>CAR</i> ; else increase <i>CAR</i>	BNC	110									
If <i>Z</i> = 0, load <i>CAR</i> , else increase <i>CAR</i>	BNZ	111									

Table 8-10 Control Information for Sequence Control Fields

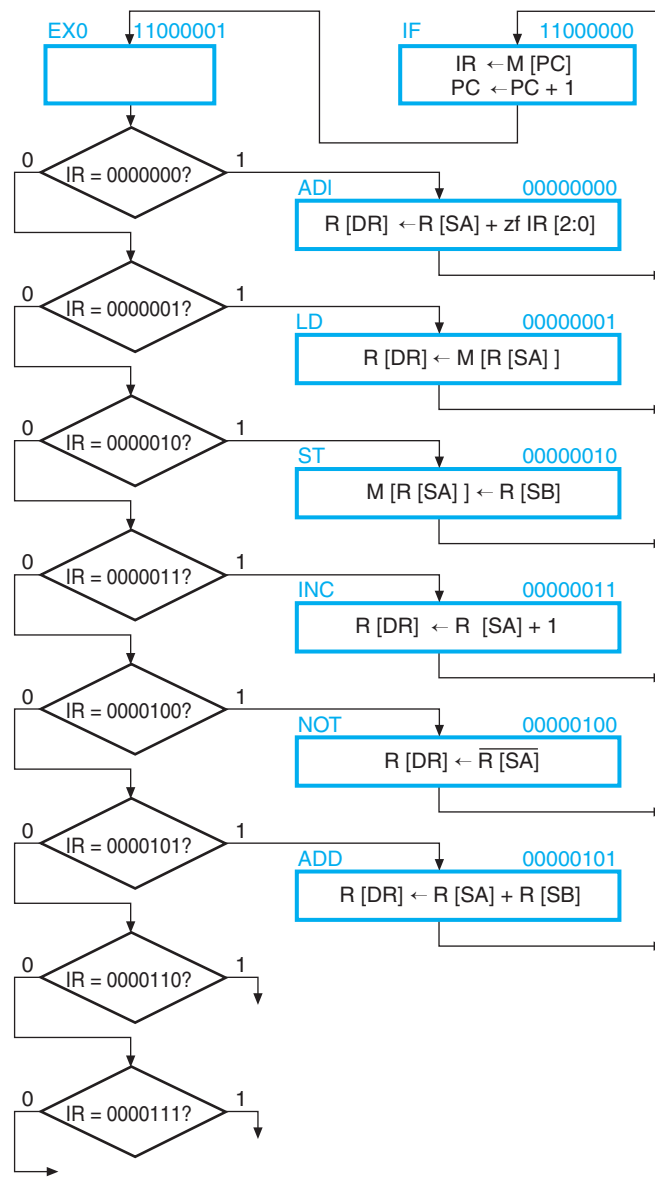


Fig. 8-28 ASM Chart for Multiple-Cycle Microprogrammed Computer

TABLE 8-11
Symbolic Microprogram for Fetch and Execution of Six Instructions

Address	NXT ADD	MS	MC	IL	PI	PL	TD	TA	TB	MB	FS	MD	RW	MM	MW
IF	EX0	CNT	—	LDI	INP	NLP	—	—	—	—	—	—	NW	PC	NW
EXO	—	NXT	OPC	NLI	NLP	NLP	—	—	—	—	—	—	NW	—	NW
ADI	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	Constant	$F = A + B$	FnUt	WR	—	NW
LD	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	—	—	Data	WR	MA	NW
ST	IF	NXT	NXA	NLI	NLP	NLP	—	SA	SB	Register	—	—	NW	MA	WR
INC	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	—	$F = \overline{A} + 1$	FnUt	WR	—	NW
NOT	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	—	—	$F = \overline{A}$	FnUt	WR	—	NW
ADD	IF	NXT	NXA	NLI	NLP	NLP	DR	SA	SB	Register	$F = A + B$	FnUt	WR	—	NW

Table 8-11 Symbolic Microprogram for Fetch and Execution of Six Instructions

TABLE 8-12
Binary Microprogram for Fetch and Execution of Six Instructions

Address	NXT ADD	MS	MC	IL	PI	PL	TD	TA	TB	MB	FS	MD	RW	MM	MW
192	193	000	0	1	1	0	0	0	0	0	00000	0	0	1	0
193	000	001	1	0	0	0	0	0	0	0	00000	0	0	0	0
000	192	001	0	0	0	0	0	0	0	1	00010	0	1	0	0
001	192	001	0	0	0	0	0	0	0	0	00000	1	1	0	0
002	192	001	0	0	0	0	0	0	0	0	00000	0	0	0	1
003	192	001	0	0	0	0	0	0	0	0	00001	0	1	0	0
004	192	001	0	0	0	0	0	0	0	0	01110	0	1	0	0
005	192	001	0	0	0	0	0	0	0	0	00010	0	1	0	0

Table 8-12 Binary Microprogram for Fetch and Execution of Six Instructions

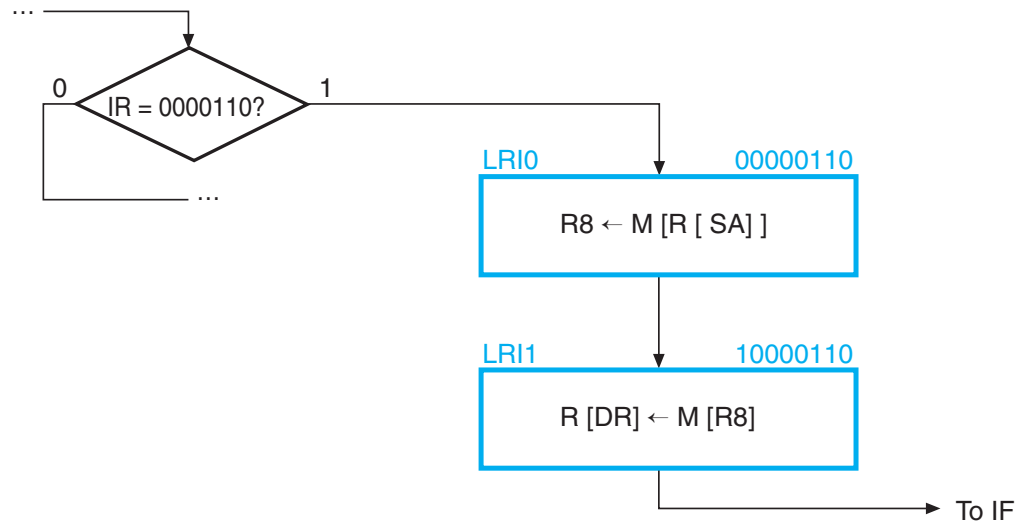


Fig. 8-29 ASM Chart for Register Indirect Instruction

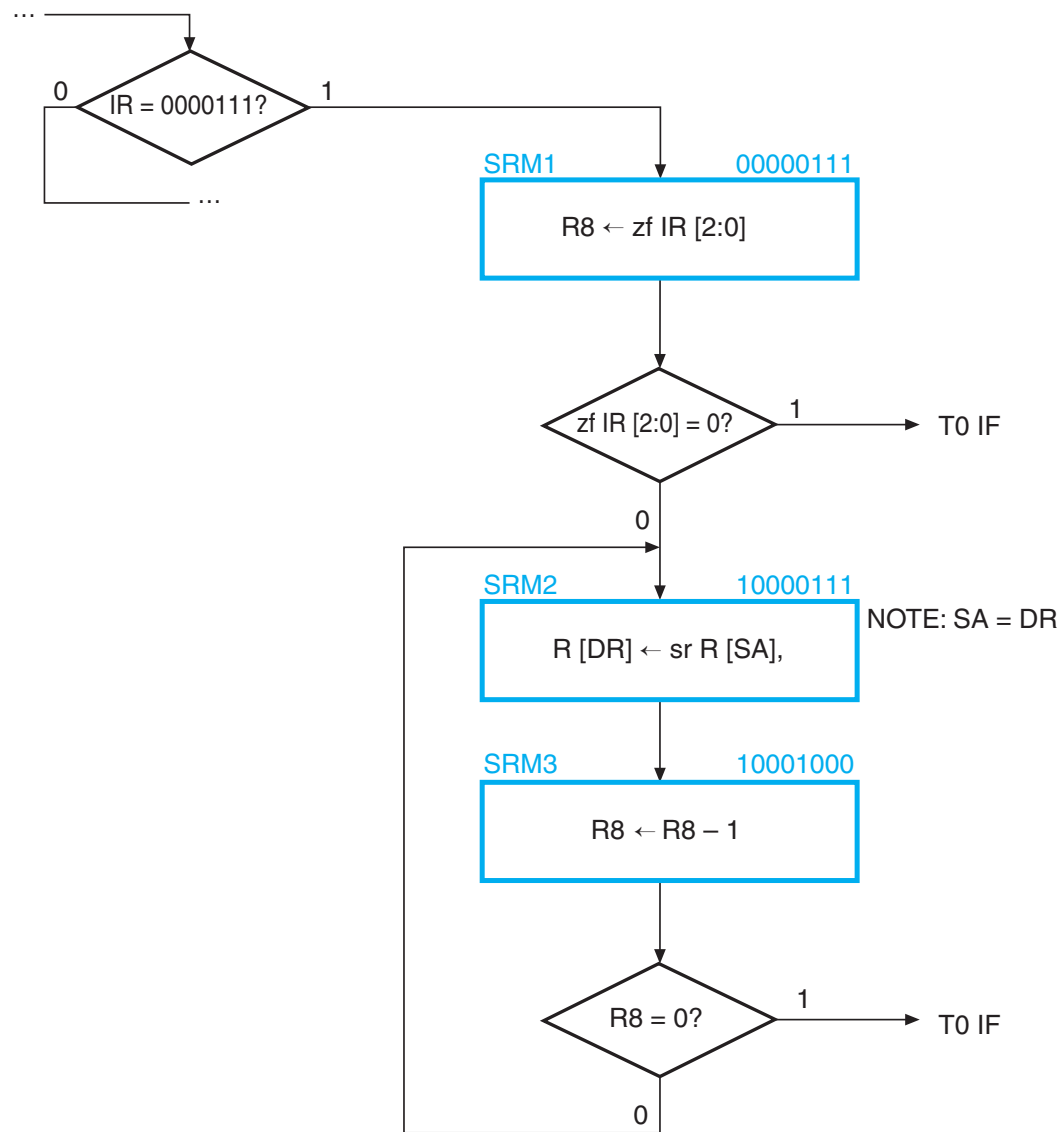


Fig. 8-30 ASM Chart for Right-Shift Multiple Instruction

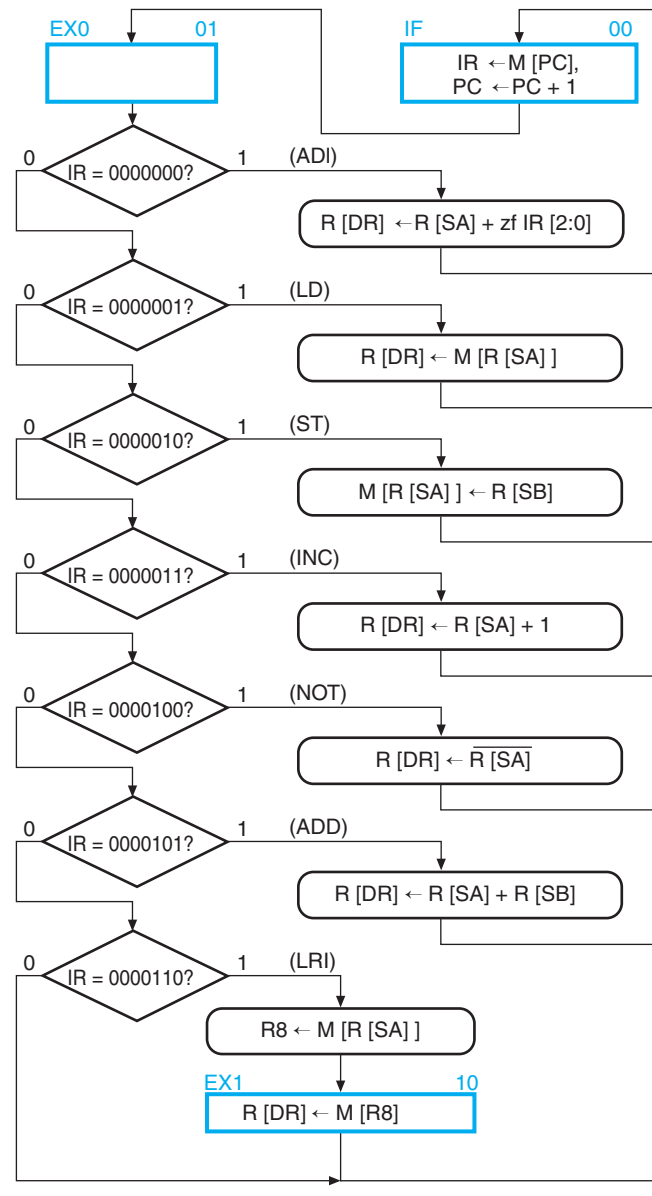


Fig. 8-31 ASM Chart for Multiple-Cycle, Decoder-Based Computer

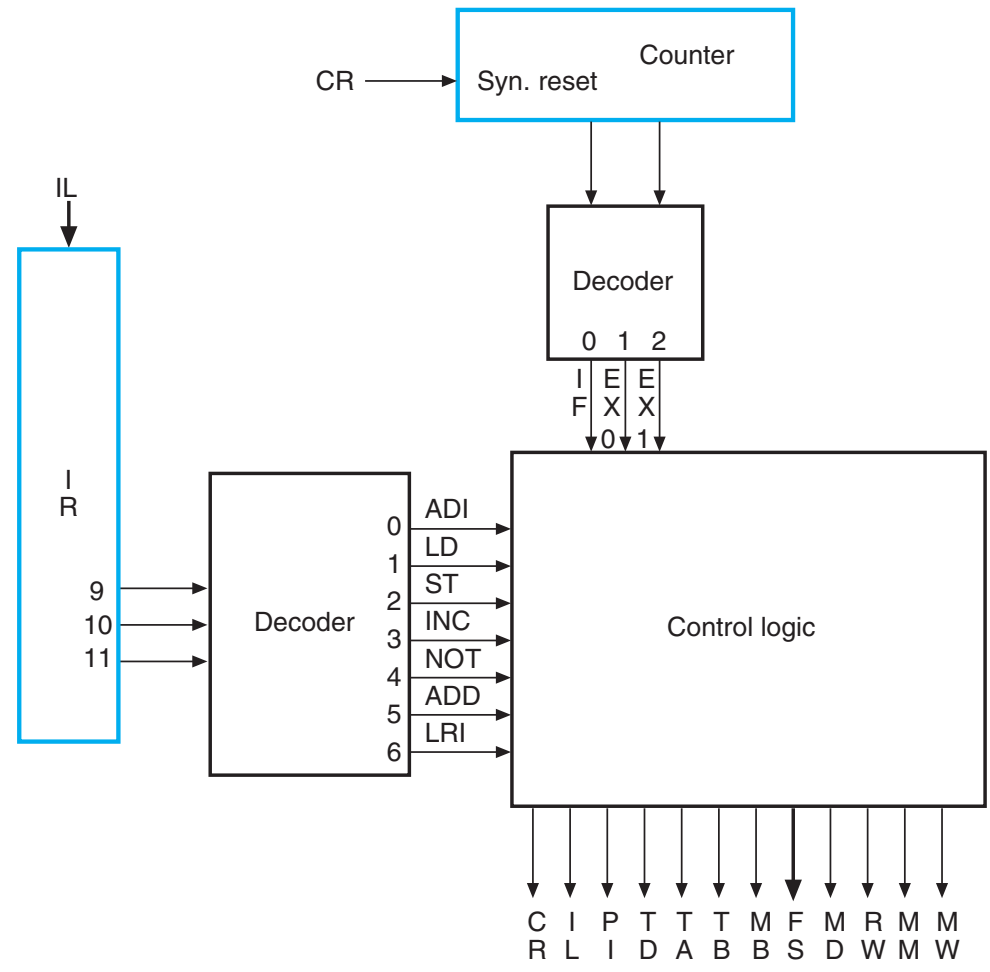


Fig. 8-32 Block Diagram of Hardwired Counter and Decoder-Based, Multiple-Cycle Control Unit



Fig. 8-33 Assembly Line Analogy to Computer Pipeline

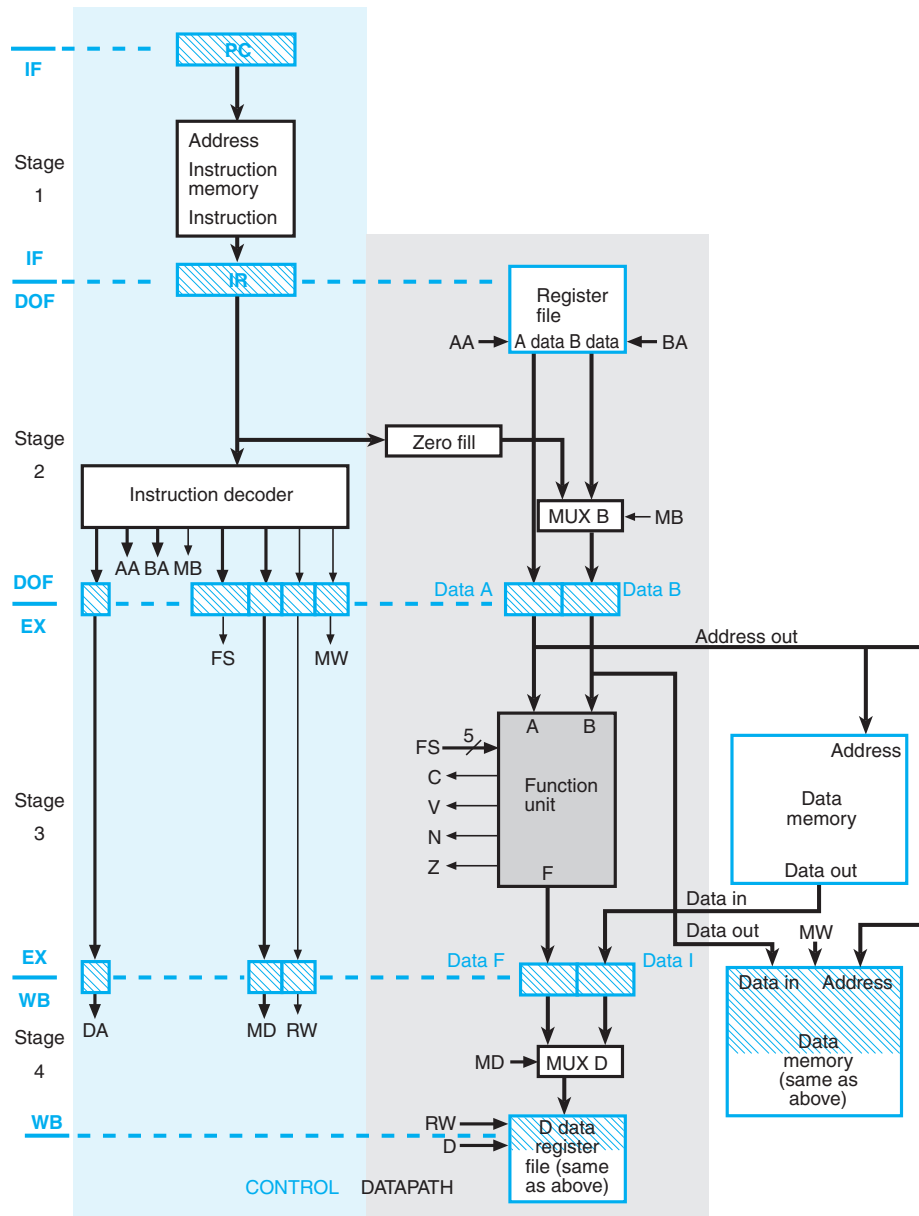


Fig. 8-34 Block Diagram of Pipelined Computer

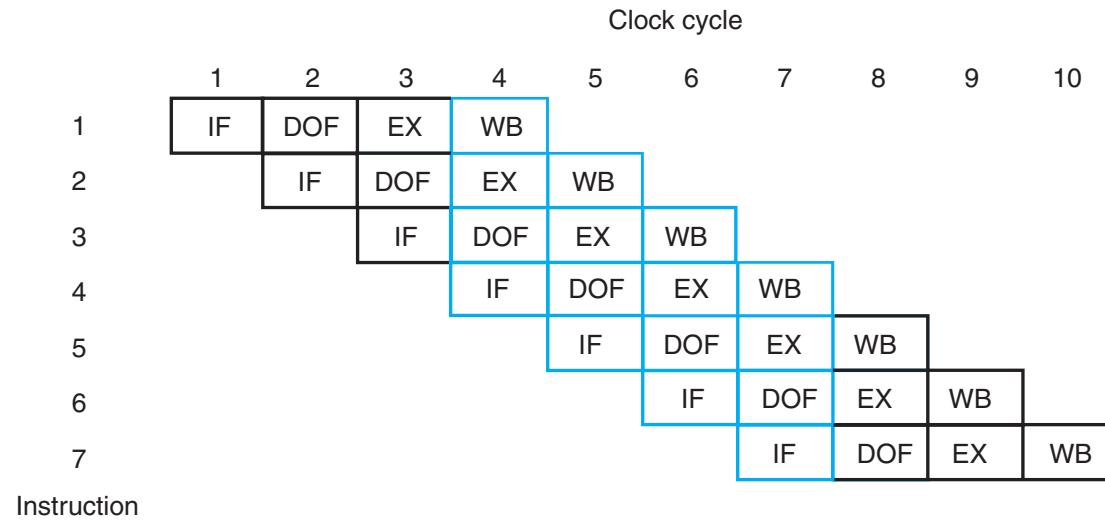


Fig. 8-35 Pipeline Execution Pattern of Register Number Program

 


Fig. 8-36 State Diagram for Problem 8-1