
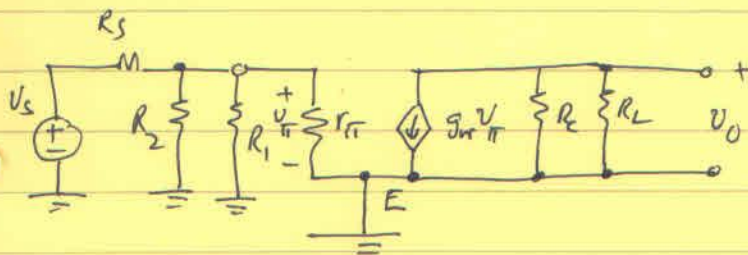


Common Emitter Amplifier

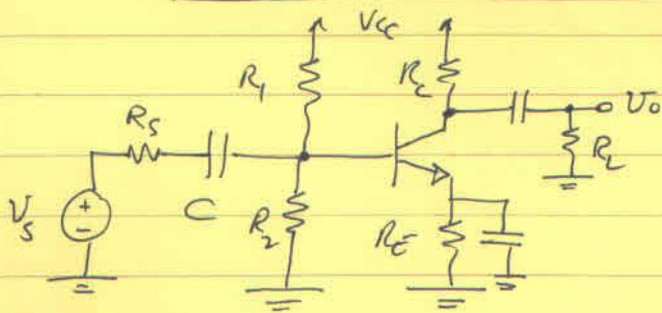

$$R_{in} = R_1 \parallel R_2 \parallel r_{\pi} = R_B \parallel r_{\pi} \quad (\text{low})$$


$$A_V = \frac{V_o}{V_{in}} = -g_m (R_c \parallel R_L) \quad (\text{Hi})$$

$$\text{and } V_{in} = V_s - i_c R_s = V_s - \left(\frac{V_{\pi}}{R_1 \parallel R_2 \parallel r_{\pi}} \right) \cdot R_s$$


$$\text{if } R_s \ll \frac{1}{R_1 \parallel R_2 \parallel r_{\pi}}$$

$$\therefore V_{in} \approx V_s$$

The Common Base Config.

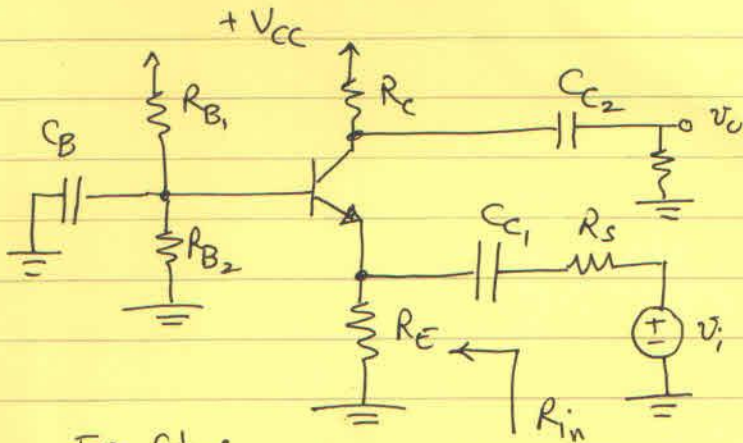

Eq. Ct.:

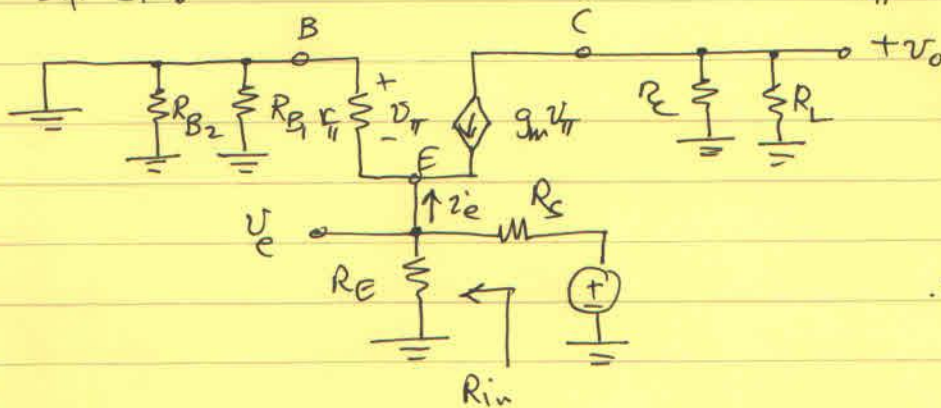

$$\frac{v_e}{v_s} = \frac{R_{in}}{R_{in} + R_s}$$

$$i_e = -\frac{v_{\pi}}{r_{\pi}} - g_m v_{\pi}$$

$$= -v_{\pi} \left(\frac{1}{r_{\pi}} + g_m \right) = -\frac{v_{\pi}}{r_e}$$

$$v_{\pi} = -v_e$$

$$\therefore \frac{v_e}{i_e} = \frac{-v_{\pi}}{-v_{\pi}/r_e}$$

$$\therefore R_{in} = R_E \parallel r_e$$

$$R_{in} \approx r_e$$


$$v_o = -g_m v_{\pi} (R_C \parallel R_L)$$

$$= g_m v_e (R_C \parallel R_L)$$


$$\therefore A_{v_{overall}} = \frac{v_o}{v_e} \cdot \frac{v_e}{v_s} = \frac{v_o}{v_s}$$

$$= g_m (R_C \parallel R_L) \cdot \frac{R_{in}}{R_{in} + R_s}$$

The Emitter follower (Common collector)

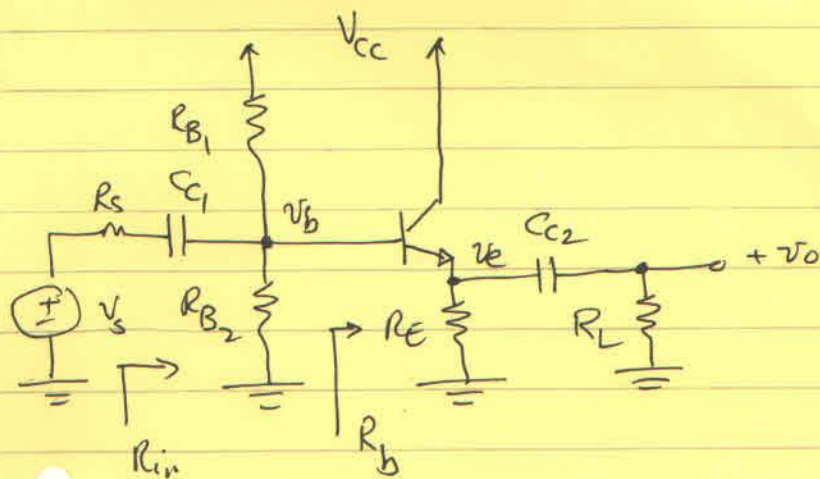

$$r_e = \frac{r_{\pi}}{1+\beta}$$

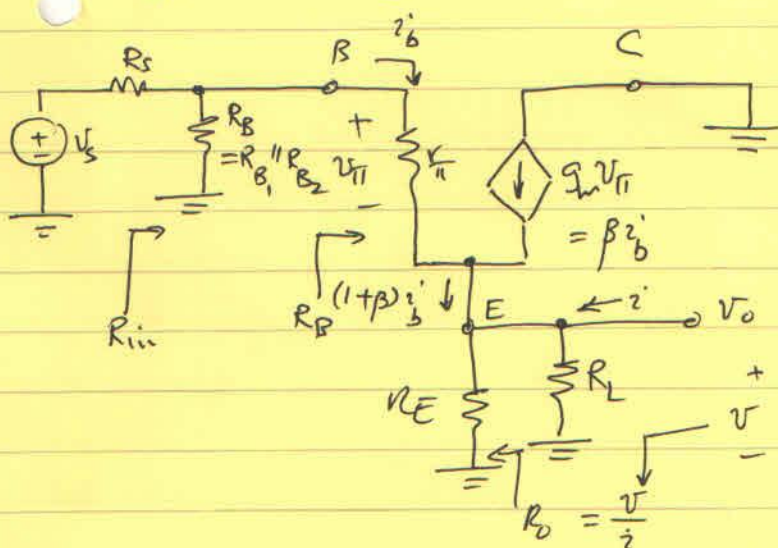

$$R_o = R_E \parallel \left[\frac{r_{\pi}}{(1+\beta)} + (R_B \parallel R_s) / (1+\beta) \right]$$

$$\therefore r_e = \frac{r_{\pi}}{1+\beta}$$

$$\therefore R_o = R_E \parallel \left[r_e + (R_B \parallel R_s) / (1+\beta) \right]$$

$$R_b = (1+\beta) \left[r_e + (R_E \parallel R_L) \right]$$

$$R_{in} = (R_{B1} \parallel R_{B2} \parallel R_b)$$

$$\frac{v_b}{v_s} = \frac{R_{in}}{R_{in} + R_s}$$

$$\frac{v_e}{v_b} = \frac{R_E \parallel R_L}{(R_E \parallel R_L) + r_e}$$

$$\therefore \frac{v_o}{v_s} = \frac{R_{in}}{R_{in} + R_s} \cdot \frac{(R_E \parallel R_L)}{(R_E \parallel R_L) + r_e}$$

The Transistor as a switch

Cut-off Region
vs.
Active Region

Cut-off Region:

If $V_{BE} < 0.5V$, the EBJ is reverse-biased and the device is in cut-off mode

$$i_B = 0, i_E = 0, i_C = 0, V_C = V_{CC}$$

Active Region

$$V_{BE} > 0.5 \approx 0.7V$$

$$V_{BE} \geq 0.7V$$

$$i_B \approx \frac{V_{BE} - 0.7}{R_B}$$

$$i_C = \beta i_B$$




$$V_C = V_{CC} - R_C i_C$$

check $V_{CE} \geq 0$?

or $V_C \geq 0$?


$V_C \geq 0.3V \therefore$ assumption correct

Transistor as Logic Inverter

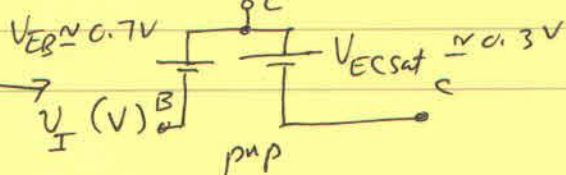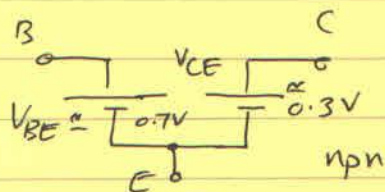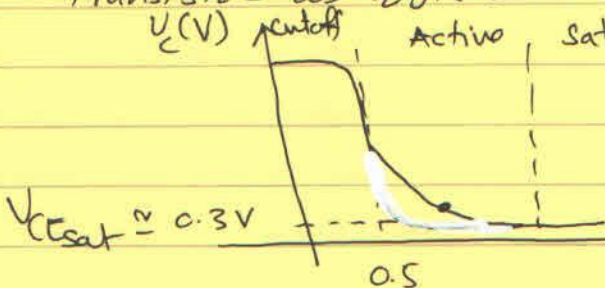

Ex. Analyze the circuit shown to determine the voltages at all nodes and the currents in all branches.

Take $\beta \geq 50$.

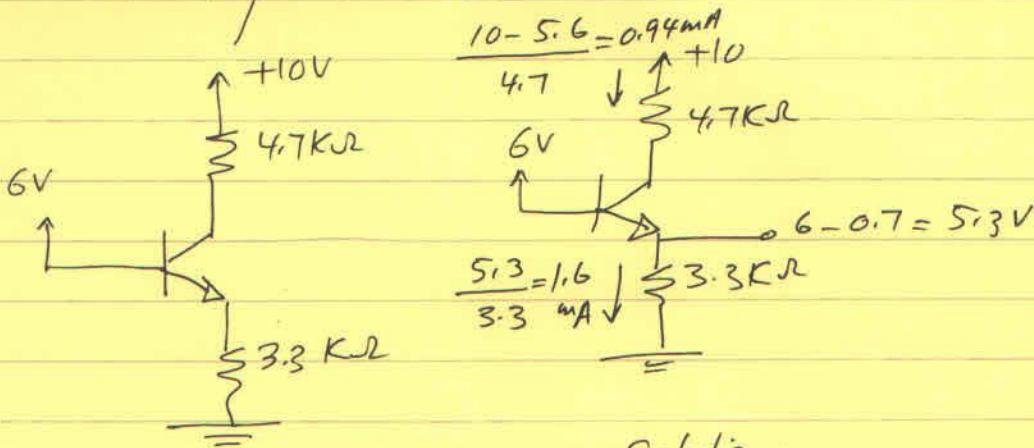

Solution!

$$V_E = 6 - 0.7 = 5.3V$$

$$V_C = V_E + V_{C_{sat}} \approx 5.3 + 0.3 = 5.6V$$

$$I_E = \frac{V_E}{3.3} = \frac{5.3}{3.3} = 1.6mA$$

$$I_C = \frac{10 - 5.6}{4.7} = 0.94mA$$

$$I_B = I_E - I_C = 1.6 - 0.94 = 0.66mA$$


$$\beta_{forced} = \frac{I_C}{I_B} = \frac{0.94}{0.66} = 1.4$$

$\therefore \beta_{forced} < \beta \therefore$ transistor is in saturation

\therefore Design based on β_{min} !

assume transistor is in saturation

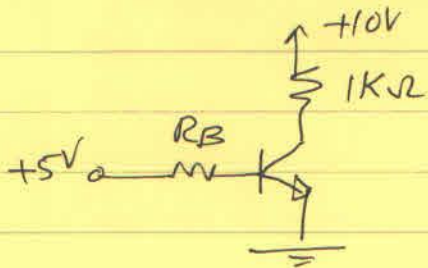Ex. If $\beta = 50 \rightarrow 150$, find the value of R_B that results in saturation with an overdrive factor of at least 10.



Solution

When saturated: $V_C = V_{CEsat} \approx 0.3V$

$$\frac{I_C}{I_{C sat}} = \frac{10 - 0.3}{1} = 9.7 \text{ mA}$$


To saturate transistor with β_{min}

$$\therefore I_{B sat} = \frac{9.7}{50} = 0.194 \text{ mA}$$

The overdrive factor of 10 $\therefore I_B = 10 \times 0.194 = 1.94 \text{ mA}$

$$\therefore R_B = \frac{5 - 0.7}{1.94} = \frac{4.3}{1.94} = 2.2 \text{ k}\Omega$$

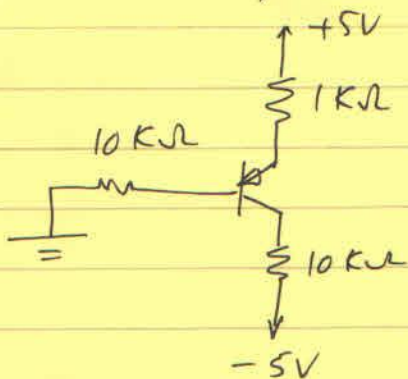Ex. $\beta_{min} = 30$, get all node voltages and all branch currents.



Solution

Transistor either in active or sat. mode.

Assume active mode & neglect base current

$$\therefore V_B \approx 0V, V_E \approx 0.7V, I_E = 4.3 \text{ mA}$$

$$I_C = 0.5 \text{ mA}$$

\therefore max

\therefore saturated transistor

$$\therefore V_E = V_B + V_{EB} \approx V_B + 0.7$$

$$V_C = V_C - V_{CEsat} \approx V_B + 0.7 - 0.3 = V_B + 0.4$$

$$I_E = \frac{5 - V_E}{1} = \frac{5 - V_B - 0.7}{1} = 4.3 - V_B \text{ mA}$$

$$I_B = \frac{V_B}{10} = 0.1 V_B$$

$$I_C = \frac{V_C - (-5)}{10} = \frac{V_B + 0.4 + 5}{10} = 0.1 V_B + 0.54 \text{ mA}$$

$$I_E = I_B + I_C$$


$$\therefore 4.3 - V_B = 0.1 V_B + 0.1 V_B + 0.54$$

$$V_B = \frac{3.76}{1.2} \approx 3.13 \text{ V}$$


$$V_E = 3.83 \text{ V}, V_C = 3.53 \text{ V}, I_E = 1.17 \text{ mA},$$

$$I_C = 0.853 \text{ mA}, I_B = 0.313 \text{ mA}$$
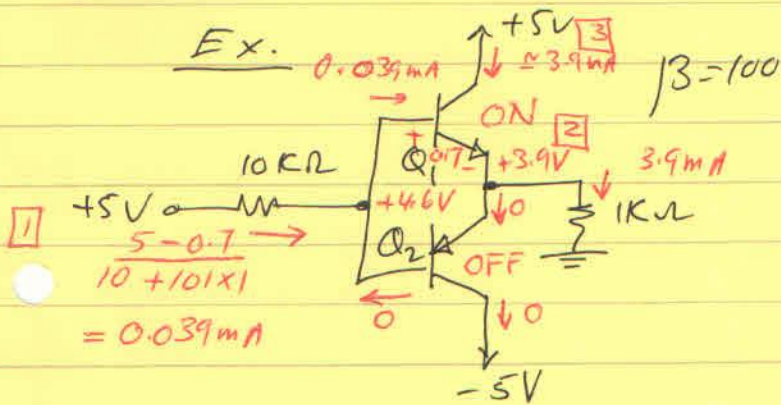
$$\beta_{\text{forced}} = \frac{0.853}{0.313} \approx 2.7 \ll \beta_{\text{min}}$$



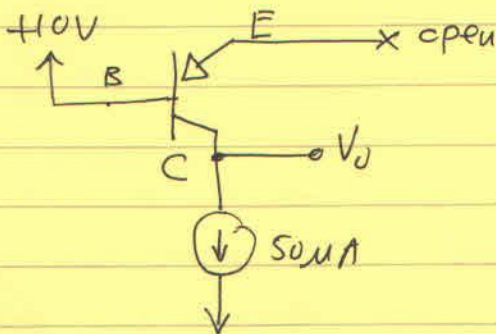Ex. $V_0 = ?$ if $V_{BCO} = 70 \text{ V} ?$



Solution

$$V_0 = V_B - V_{BCO} = 10 - 70 = -60 \text{ V}$$