

Ex. (On Operational Amplifiers)

The circuit shown represents a simple operational amplifier. Terminals 1, 2 connected to the ground are the op amp's input terminals and terminal 3 is the output terminal.  $Q_6$  has 4 times the area of each  $Q_9, Q_3$ .

(a) Perform an approximate dc analysis ( $\beta \gg 1$ ) to calculate the dc currents & voltages at all branches and nodes

Hint:  $Q_6$  carry 4 times the collector current of either  $Q_9$  or  $Q_3$ !

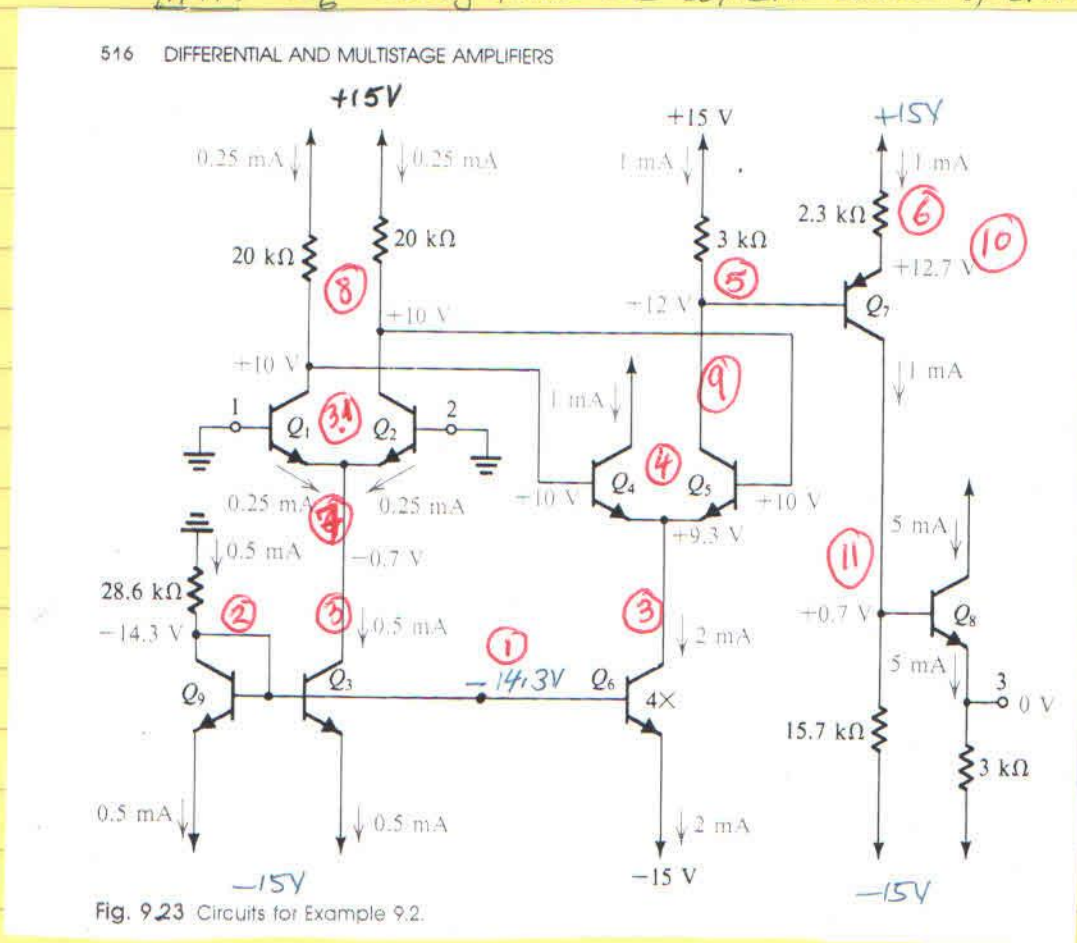


Fig. 9.23 Circuits for Example 9.2.

Solution

① Voltage at Base of  $Q_6$  is  $-15 + 0.7 = -14.3V$   
same as collector voltage of  $Q_9$

②  $\therefore I_{CQ9} = \frac{0 - (-14.3)}{28.6} = 0.5 \text{ mA}$

③  $\therefore Q_1, Q_2$  conducts  $\frac{0.5}{2} = 0.25 \text{ mA}$   
 $\therefore V_{CQ1} = V_{CQ2} = 15 - 20(0.25) = 10V$   
 $\therefore V_{BQ4} = V_{BQ5} = 10V \therefore V_{E Q4} = 9.3V$

③  $Q_3$  conducts  $0.5 \text{ mA}$  & accordingly  $Q_6$  conducts  $(4(0.5)) = 2 \text{ mA}$

④\*  $Q_4, Q_5$  conducts  $1 \text{ mA}$  each

⑤  $\therefore V_{CQ5} = 15 - 1(3) = 12V = V_{BQ7} \therefore V_{E Q7} = 12 + 0.7 = 12.7V$

$$(6) \therefore I_{EQ2} = \frac{15 - 12.7}{2.3} = 1 \text{ mA}$$

$$I_{CQ5} = I_{CQ4} = \frac{15 - 12}{3} = 1 \text{ mA}$$

Also from symmetry, since  $I_{CQ3} = 0.5 \text{ mA}$ , then  $\frac{I_{CQ2}}{I_{EQ2}} = \frac{I_{EQ1}}{I_{EQ1}} = \frac{0.5}{2}$   
 $= 0.25 \text{ mA}$

$$(7) V_{EQ2} = V_{EQ1} = 0 - 0.7 = -0.7 \text{ V}$$

$$\text{Since } \frac{I_{CQ2}}{I_{EQ2}} = \frac{I_{CQ1}}{I_{EQ1}} = \frac{I_{CQ1}}{I_{EQ1}} = 0.25 \text{ mA}$$

$$(8) \therefore V_{CQ1} = V_{CQ2} = 15 - 0.25(20) = 10 \text{ V}$$

$$\therefore V_{EQ4} = V_{EQ5} = 10 - 0.7 = 9.3 \text{ V}$$

$$(9) \text{ since } V_{CQ5} = 12 \text{ V} = V_{BQ7}$$

$$\therefore V_{EQ7} = 12.7 \text{ V}$$

$$(10) \therefore I_{EQ7} = \frac{15 - 12.7}{2.3} = 1 \text{ mA}$$

$$\therefore V_{BQ8} = -15 + 15.7(1) = 0.7 \text{ V}$$

(11)

$$\therefore V_{EQ8} = 0.7 - 0.7 = 0 \text{ V}$$

$$\therefore I_{EQ1} = \frac{15}{3} = 5 \text{ mA}$$